

Waveform Generators


- In the design of electronic systems, the need for signals having standard waveforms - sinusoidal, square, triangular, or pulse.
- Systems like computer and control systems require standard signals i.e. clock pulses are needed for timing.
- Communication systems where signals of a variety of waveforms are utilized as information carriers.
- Test and measurement systems where signals, a variety of waveforms, are employed for testing and characterizing electronic devices and circuits.

Waveform Generators

- Sinusoidal Waveform
 - for the generation of sinusoids a **positive-feedback loop** consisting of an amplifier and an RC **frequency-selective network**.
- Generating square, triangular, pulse (etc.) waveforms
 - employ circuit building blocks known as **multivibrators**.
 - They are three types : the **bistable**, the **astable**, and the **monostable**.

Basic Principles of Sinusoidal Oscillators

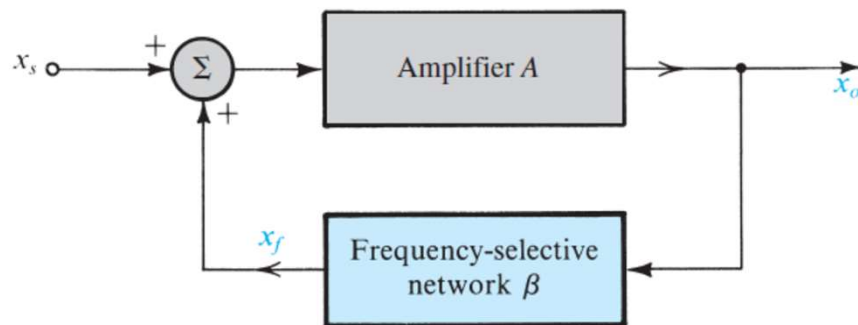- The basic structure of a sinusoidal oscillator consists of an amplifier and a frequency-selective network connected in a **positive-feedback loop**



$$x_o = A(x_s + x_f) \quad x_f = \beta x_o$$

$$x_o = A(x_s + \beta x_o) \quad x_o(1 - A\beta) = Ax_s$$

$$\frac{x_o}{x_s} = \frac{A}{(1 - A\beta)} = A_f$$

$$A_f(s) = \frac{A(s)}{1 - A(s)\beta(s)}$$

$$L(s) \equiv A(s)\beta(s)$$

Condition for Oscillation

- The characteristic equation is

$$1 - L(s) = 0$$


- If at a specific frequency f_0 the loop gain $L = A\beta$ is equal to unity, it follows from that A_f will be infinite.
- That is, at this frequency the circuit will have a finite output for zero input signal. Such a circuit is called as “Oscillator”.
- Thus the condition for the feedback loop to provide sinusoidal oscillations of frequency ω_0 is

$$L(j\omega_0) \equiv A(j\omega_0)\beta(j\omega_0) = 1$$

Wien-Bridge Oscillator

- The circuit consists of an op amp connected in the noninverting configuration, with a closed-loop gain of $A = 1 + R_2/R_1$.
- In the feedback path, RC network is connected
- Feedback factor β is given by,
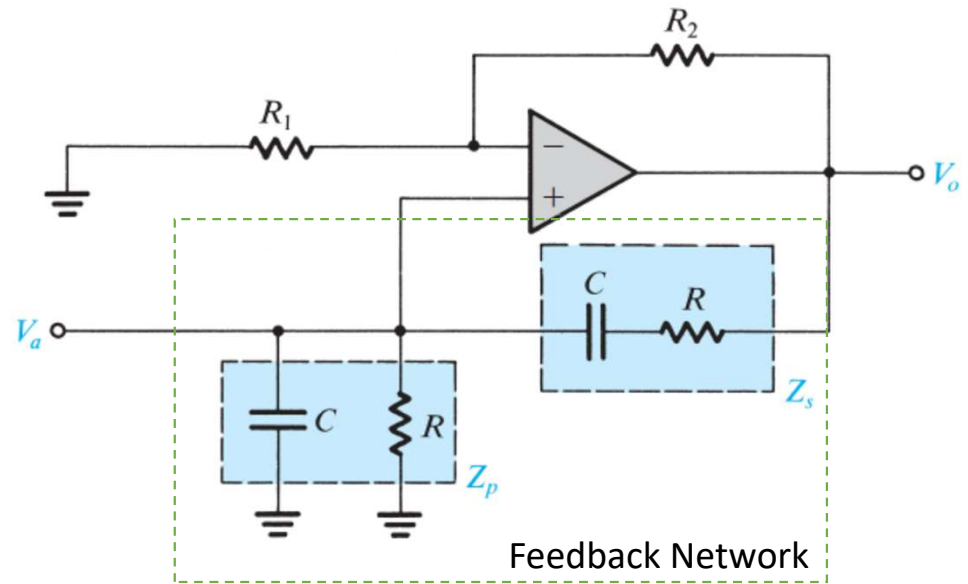
$$\beta = \frac{V_a}{V_o} = \frac{Z_p}{Z_p + Z_s}$$



Analysis

- Impedance of the RC parallel combination
- Impedance of the RC series combination
- Hence the feedback factor is

$$Z_p = \frac{1}{Y_p} = \frac{1}{\frac{1}{R} + j\omega C} = \frac{R}{1 + j\omega RC}$$

$$Z_s = \frac{1}{j\omega C} + R = \frac{1 + j\omega RC}{j\omega C}$$

$$\beta = \frac{Z_p}{Z_p + Z_s} = \frac{j\omega RC}{1 - (\omega RC)^2 + j3\omega RC}$$

$$Z_p + Z_s = \frac{1 - (\omega RC)^2 + j3\omega RC}{j\omega C(1 + j\omega RC)}$$

Analysis

- For the circuit to have oscillations,

$$A\beta = 1$$

- Since A is a real quantity, β must also be a real quantity, hence

$$1 - (\omega RC)^2 = 0$$

- Thus the frequency of oscillation is, $f = \frac{1}{2\pi RC}$


- Then $\beta = 1/3$, leading to $A = 3$, (since $A = 1 + R_2/R_1$), $R_2 = 2R_1$.

Example:

- Determine the maximum and minimum frequency of oscillations of a **Wien Bridge Oscillator** circuit having a resistor of $10\text{k}\Omega$ and a variable capacitor of 1nF to 1000nF .

Regenerative Comparator

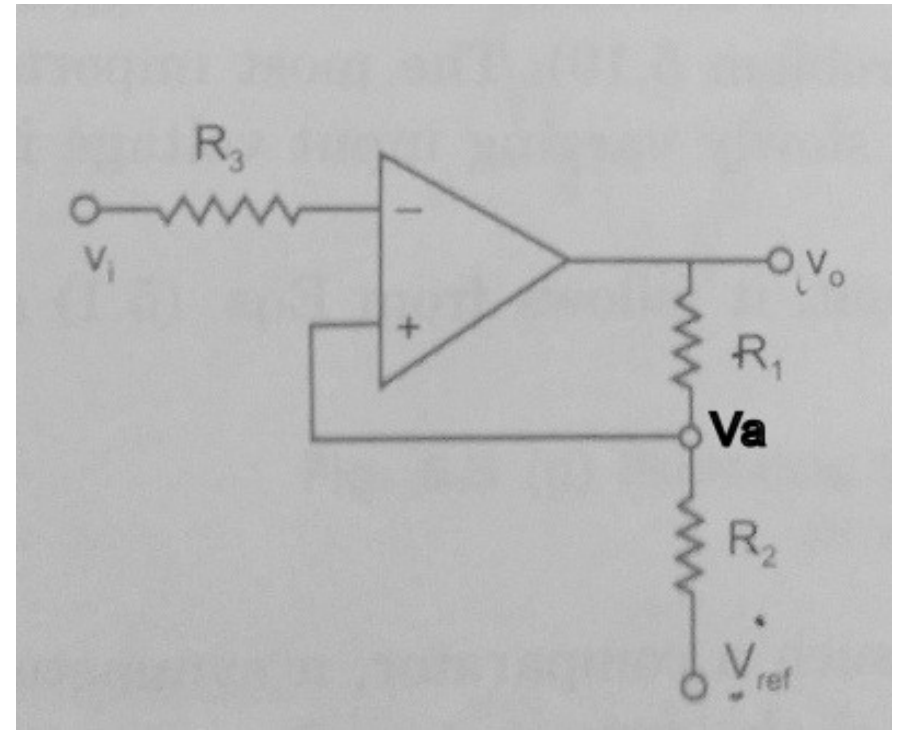- V_i applied at (-) input terminal and feedback voltage to the (+) input terminal.
- V_i triggers the output V_o every time it exceeds the certain voltage level.
- The voltage levels are called upper (lower) threshold voltage V_{UT} (V_{LT}).
- $V_{UT} - V_{LT}$ is referred as hysteresis width



Computing Upper Threshold voltages (V_{UT})

- Let $V_o = +V_{sat}$: to determine 'Va' i.e. V_{UT} , use superposition

- Case 1: Assuming $V_{ref} = 0$, voltage across " R_2 " will be V_a ,

$$V_a = V_{UT} = \frac{R_2}{R_1 + R_2} V_{sat}$$

- Case 2: By considering $V_o = 0$, then voltage across R_1 will be V_a

$$V_a = \frac{R_1}{R_1 + R_2} V_{ref}$$

- By combining the above two cases,

$$V_{UT} = \frac{R_1}{R_1 + R_2} V_{ref} + \frac{R_2}{R_1 + R_2} V_{sat}$$

Computing Lower Threshold voltage (V_{LT})

- Let $V_o = -V_{sat}$: to determine ' V_a ' i.e. V_{LT} , again use superposition
- Case 1: Assuming $V_{ref} = 0$, voltage across " R_2 " will be,

$$V_a = -\frac{R_2}{R_1 + R_2} V_{sat}$$



- Case 2: By considering $V_o = 0$, then voltage across R_1 will be,

$$V_a = \frac{R_1}{R_1 + R_2} V_{ref}$$

- By combining the above two cases,

$$V_{LT} = \frac{R_1}{R_1 + R_2} V_{ref} - \frac{R_2}{R_1 + R_2} V_{sat}$$


Asymmetric Square wave

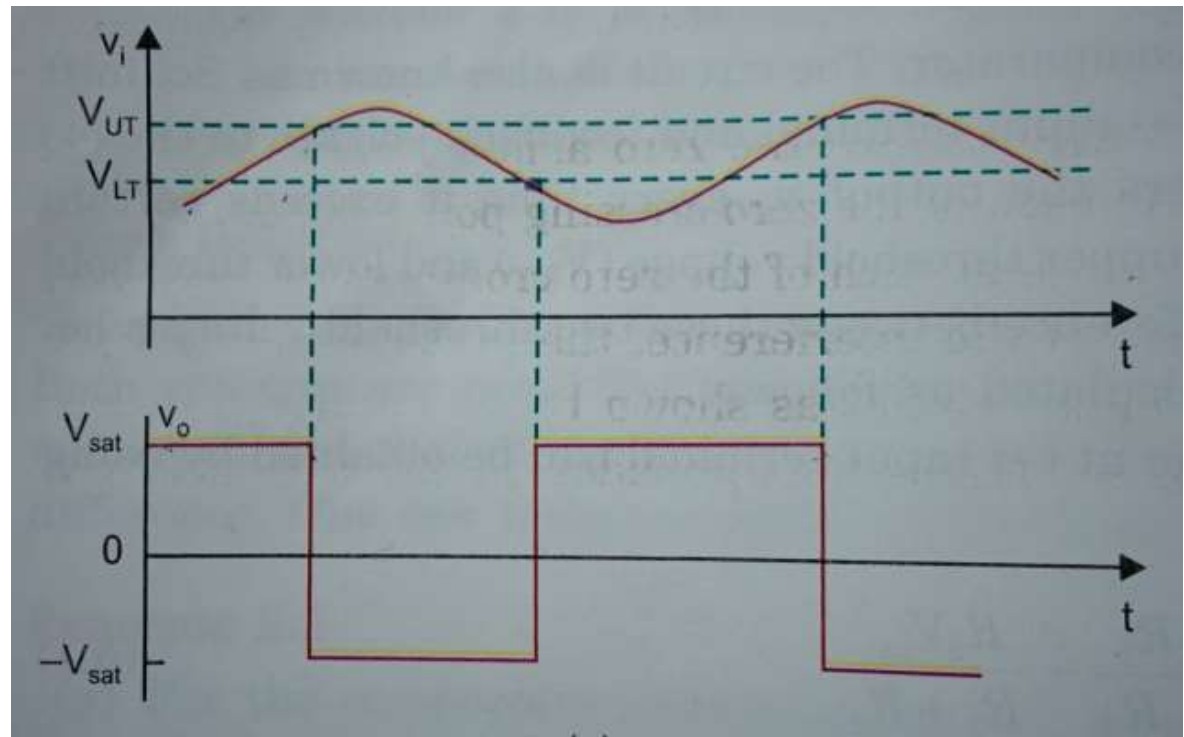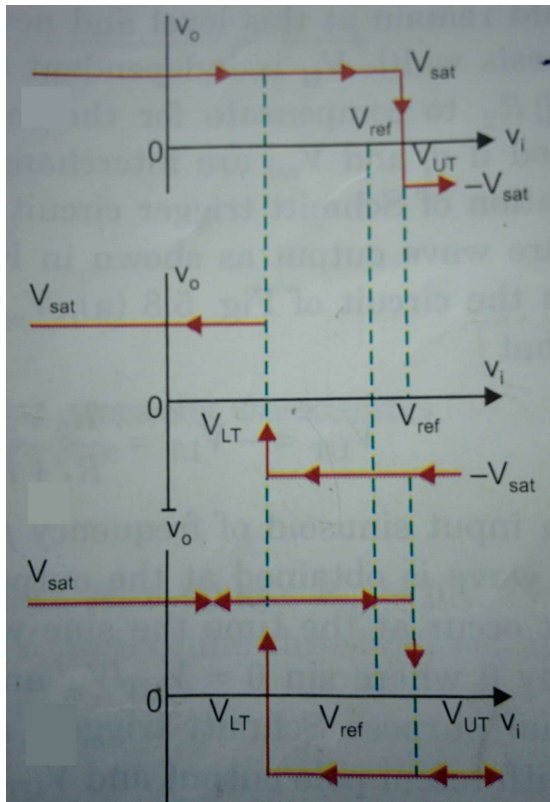

- Hysteresis width is

$$V_H = \frac{2R_2}{R_1 + R_2} V_{sat}$$

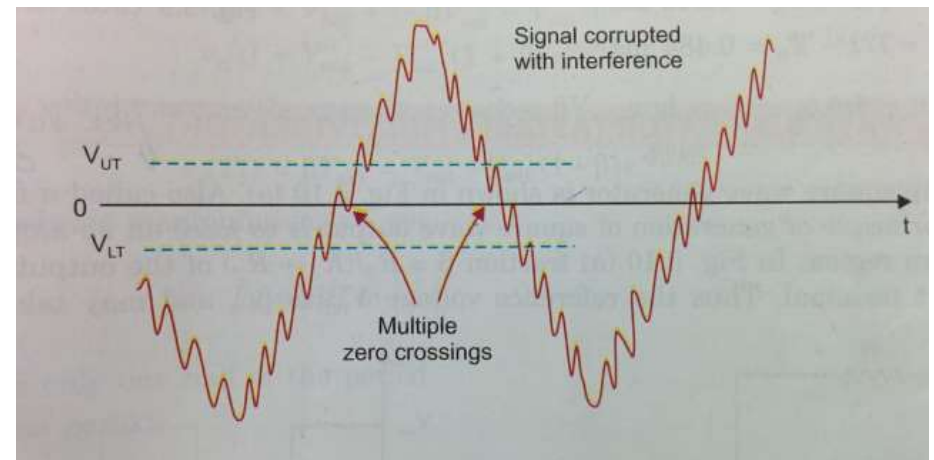- Further, if the ref voltage is zero, then symmetric square wave can be obtained.
- Application:
 - slow varying input can be converted in square wave output.
 - Superior to simple zero crossing detector circuit.



Example:

- In the given circuit of Schmitt trigger, $R_2 = 100 \Omega$, $R_1 = 50 \text{ K}\Omega$, $V_{\text{ref}} = 0 \text{ V}$, $V_i = 1 \text{ Vpp}$ sine wave and saturation voltage = $\pm 14 \text{ V}$. Determine the threshold voltages V_{UT} , V_{LT} and V_H .

$$V_{UT} = +\frac{R_2}{R_1 + R_2} V_{sat} = 28 \text{ mV}$$

$$V_{LT} = -\frac{R_2}{R_1 + R_2} V_{sat} = -28 \text{ mV}$$

$$V_H = \frac{2R_2}{R_1 + R_2} V_{sat} = 56 \text{ mV}$$