

# BASIC ELECTRONIC CIRCUITS

Bipolar Junction Transistor

# Contents



- Types of Transistors: Bipolar and field effect.
- Physical construction
- Modes of Operation
- Types of Configurations
- Input/output characteristics
- Application as an Amplifier

# Introduction

- BJT - A three terminal device.
- Applications includes, signal amplification, design of logic circuits and memory circuits
- The basic principle involved is the use of the voltage between two terminals to control the current flowing in the third terminal.
- The control signal can be used to cause the current in the third terminal to change from zero to a large value, thus allowing the device to act as a switch.
- The BJT remains popular in discrete-circuit design, where it is used together with other discrete components such as resistors and capacitors to implement circuits that are assembled on printed-circuit boards (PCBs).

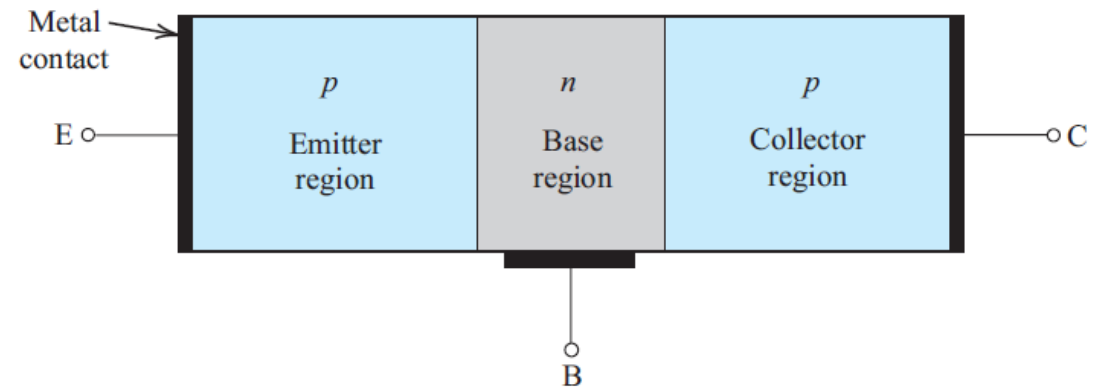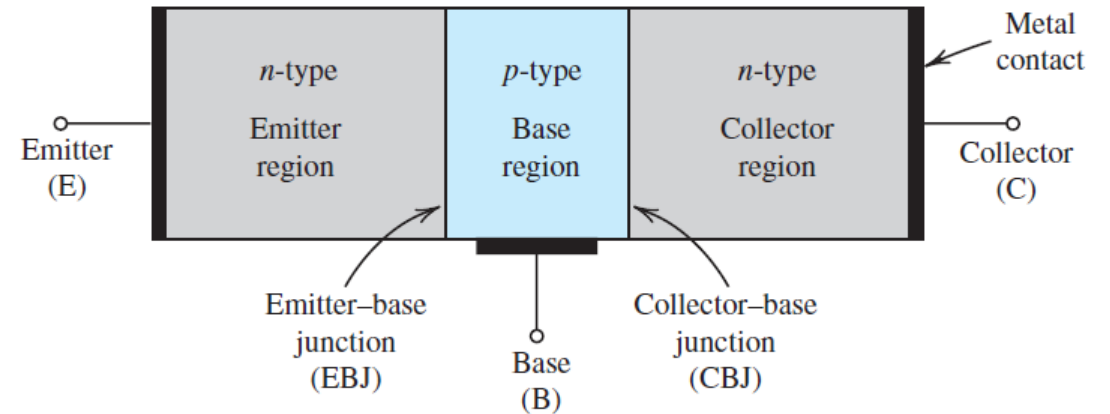
# Simplified Structure

- electrons and holes—participate in the current-conduction process in a bipolar transistor, which is the reason for the name *bipolar*
- The transistor consists of two *pn* junctions, the **emitter-base junction (EBJ)** and the **collector-base junction (CBJ)**.




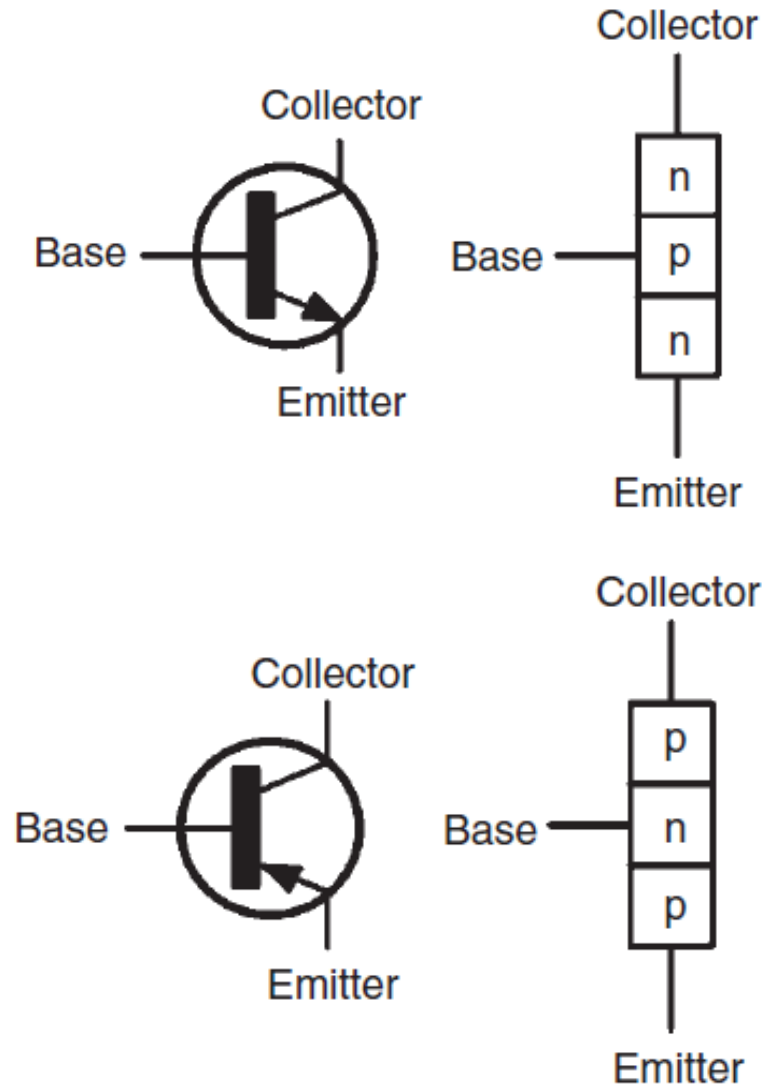
# BJT: Symbols and junction models



- Emitter - Medium sized and heavily doped, to inject majority carriers to collector through Base.
- Collector - Thick and lightly doped, designed to collect the majority carriers from emitter.
- Base - Thin and medium doped, control the flow of current between Emitter and Collector.




# BJT: Physical Construction

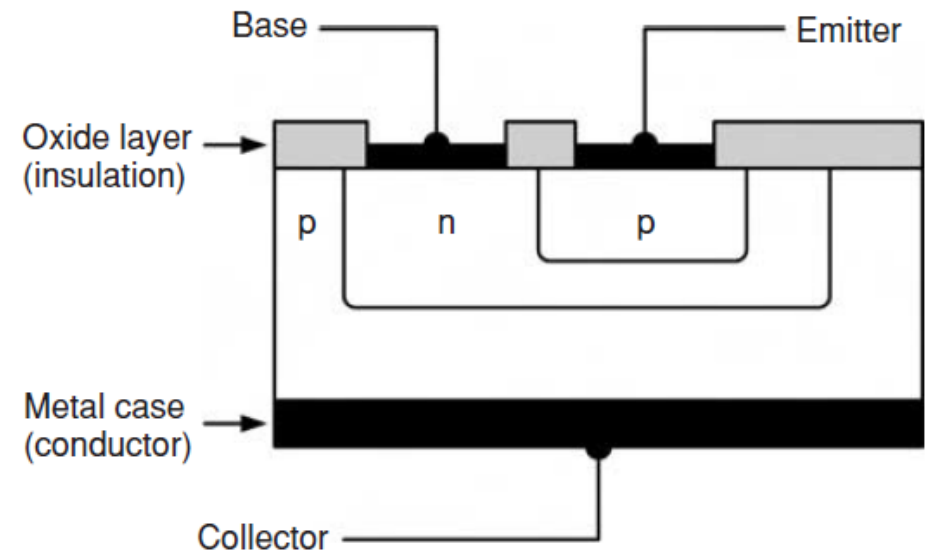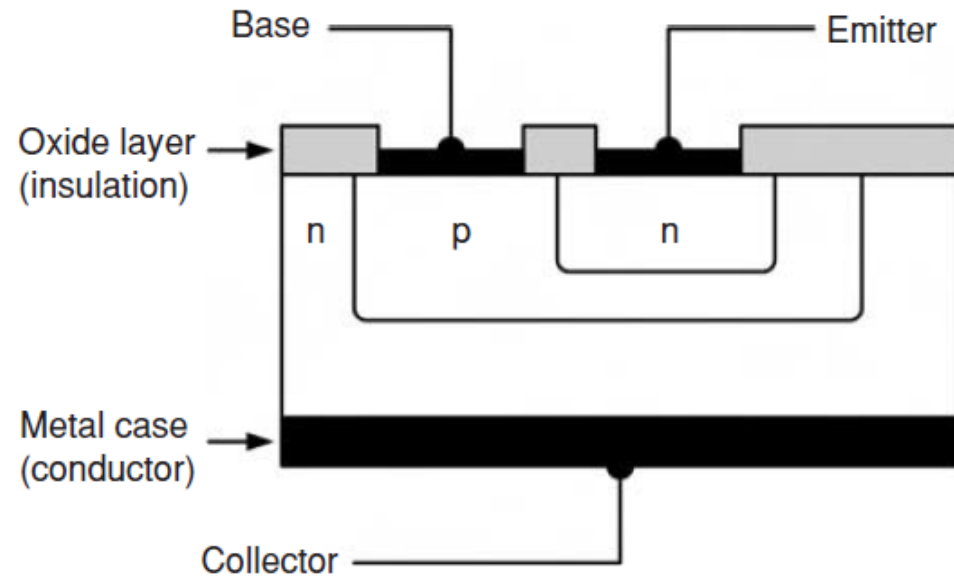

# BJT: Modes of Operation

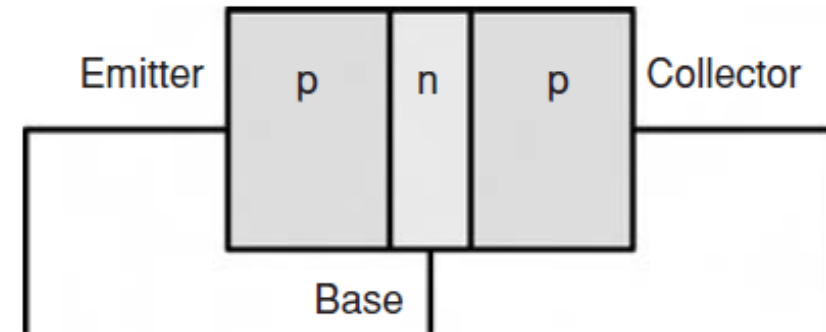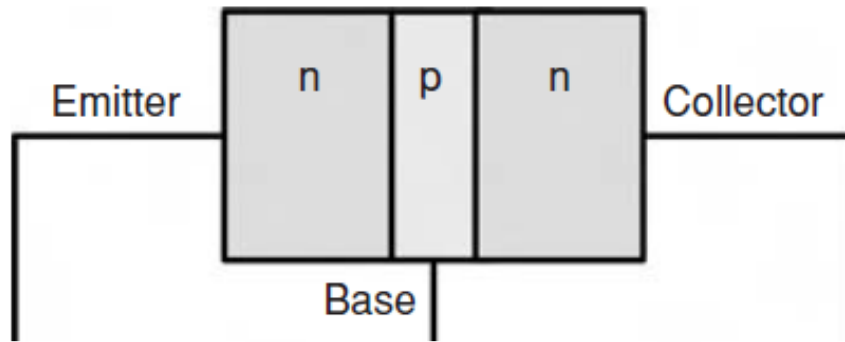


S. No.	Mode	Emitter-Base Junction	Collector Base Junction	Action	Application
1	Cut-off	Reverse	Reverse	Open	Switch
2	Saturation	forward	forward	Short	
3	Active	Forward	Reverse		Amplifier
4	Reverse active	Reverse	Forward		

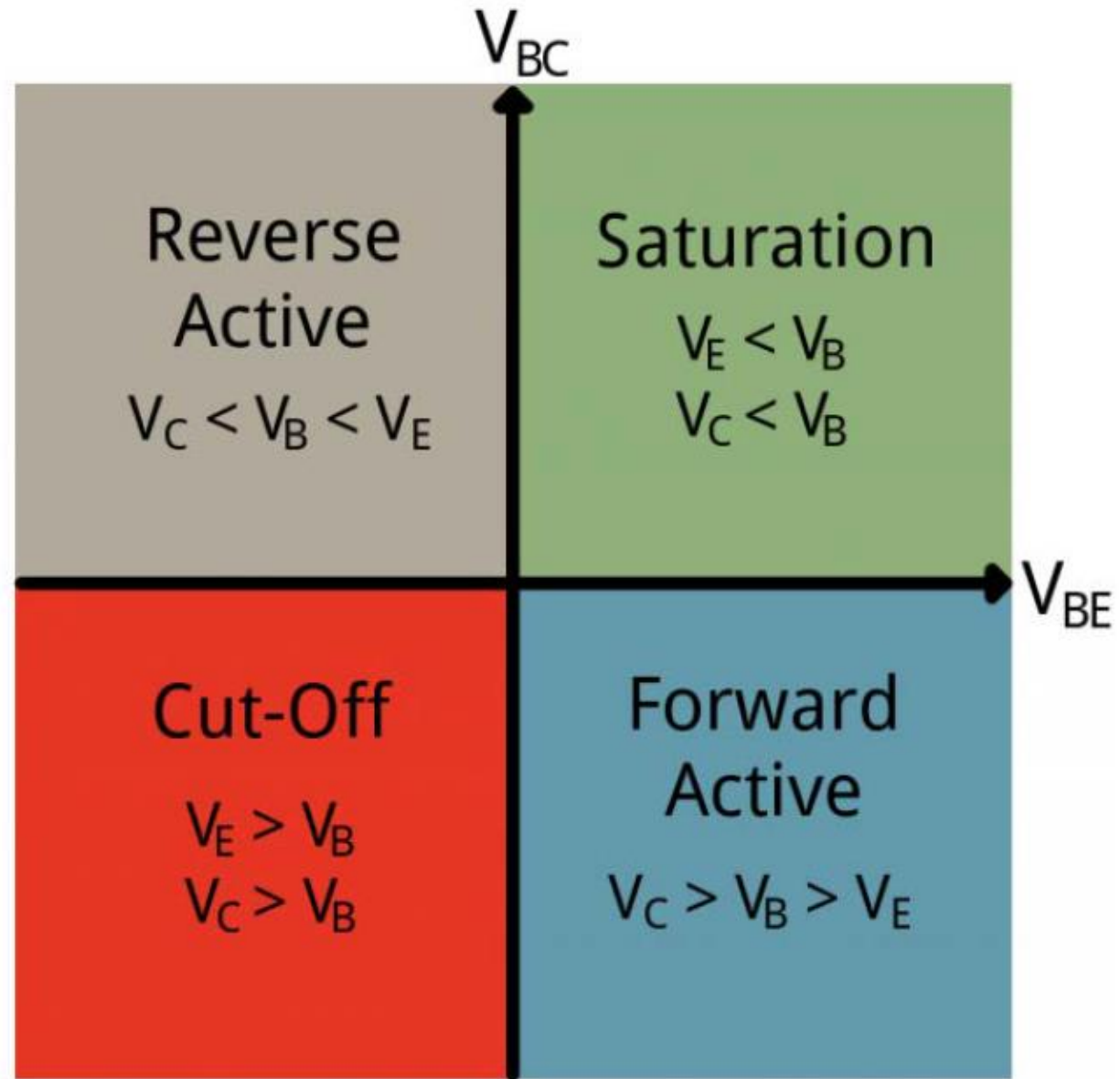




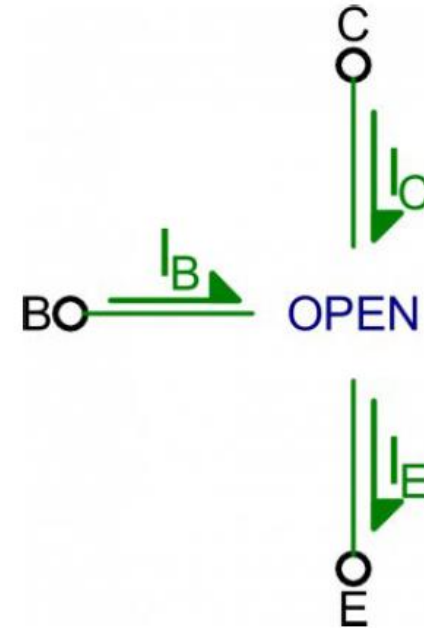- Cut-off Mode:
- No collector current and no emitter current.
- Very much like a open circuit



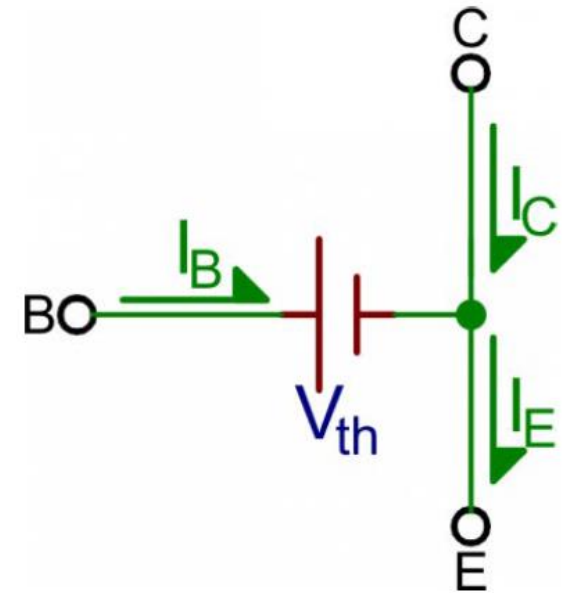- Saturation mode: on state
- Acts like a short circuit between the collector and emitter.
- Both the junctions are forward biased,  $V_B$  must be at higher potential than  $V_C$  and  $V_E$ .
- $V_C$  must be slightly greater than  $V_E$ .
- $V_{CE} = 0.2 \text{ V}$ .




- Active Mode:
- $V_{BE}$  must be positive and  $V_{CB}$  must be negative.  $V_C > V_B > V_E$ .
- Gain (amplification factor) -  $\beta$
- Common base current gain -  $\alpha$

$$I_C = \beta I_B$$

$$I_C = \alpha I_E$$


$$\beta = \frac{\alpha}{(1-\alpha)}$$

$$\alpha = \frac{\beta}{\beta+1}$$

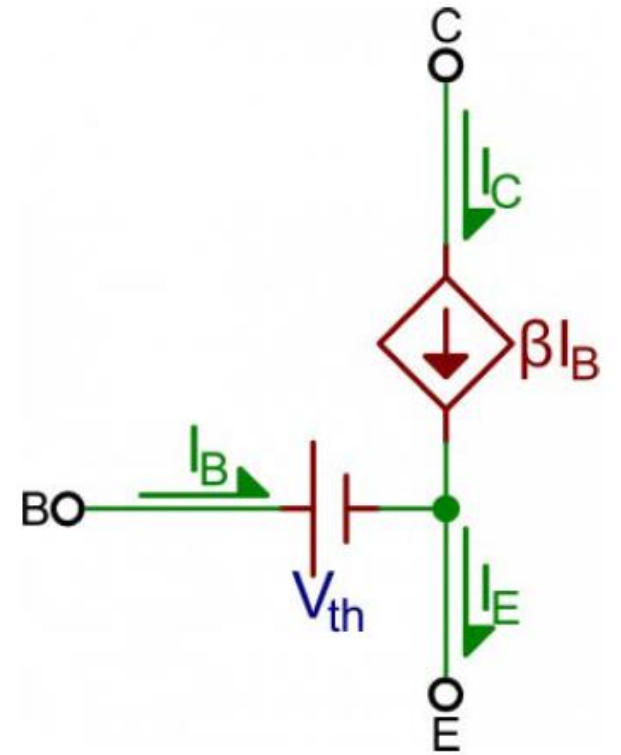

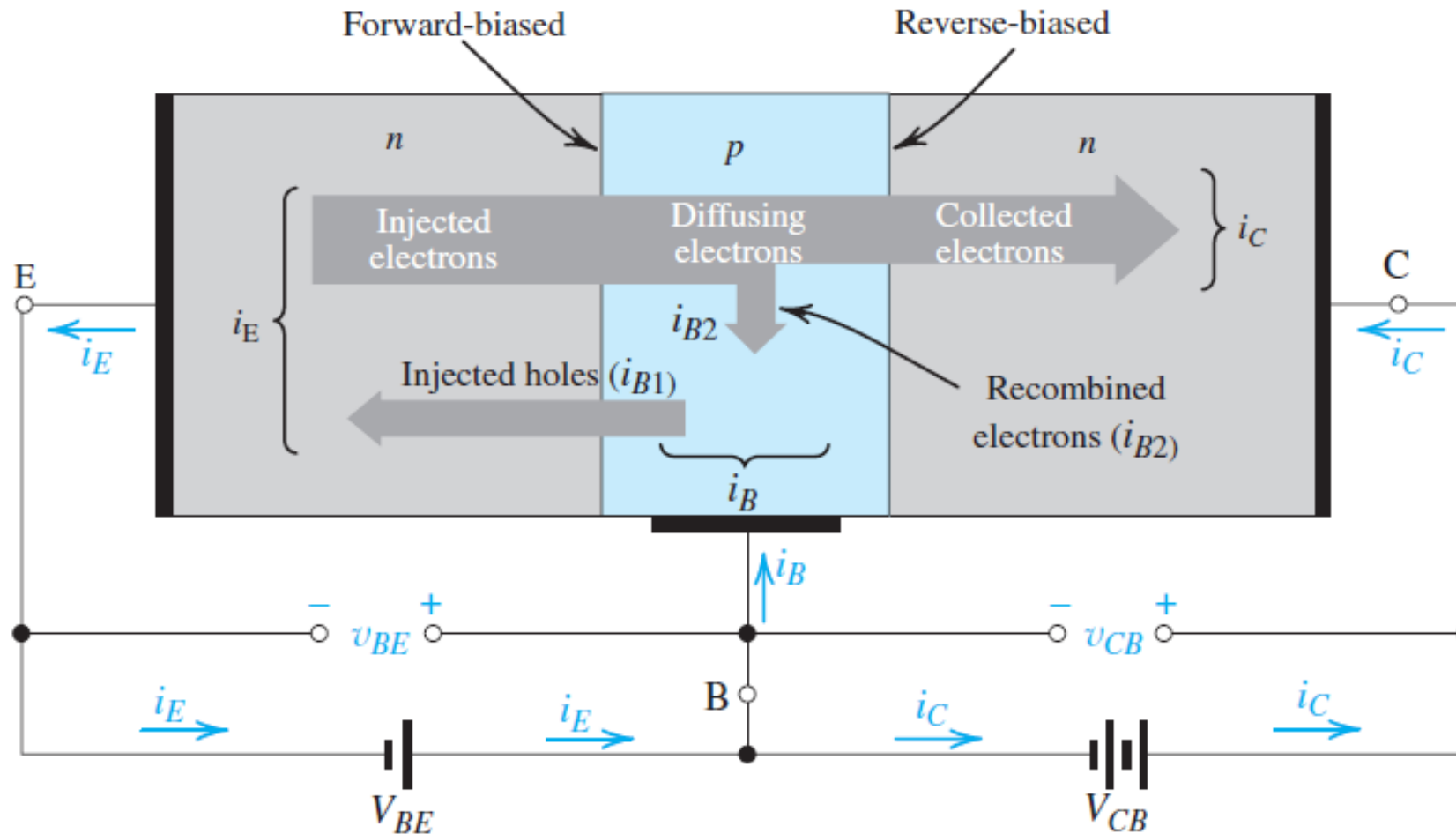
# Transistor Action: Active mode

- Emitter-Base junction is Forward Biased, Collector-Base junction is Reverse Biased



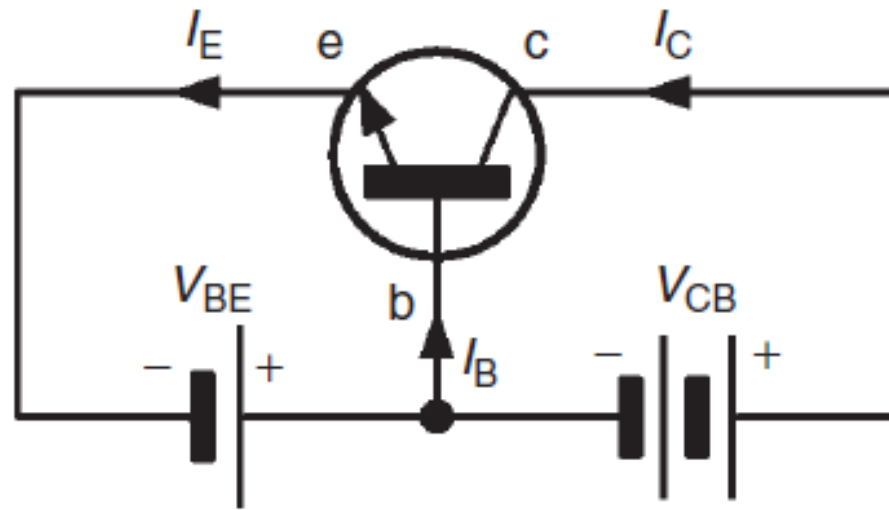
# BJT: Bias and Current Flow

- For linear amplification, BE junction is forward bias and CE junction is reverse biased.
- Base region is made very small such that the carriers are swept across it from emitter to collector.



$$I_E = I_B + I_C$$

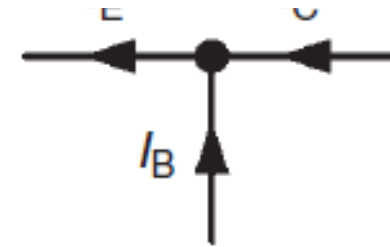


$$I_C = \beta I_B \quad I_C = \alpha I_E$$

$$\beta = \frac{\alpha}{(1-\alpha)}$$
$$\alpha = \frac{\beta}{\beta+1}$$


The transistor in the circuit of Figure has  $\beta = 100$  and exhibits a  $v_{BE}$  of 0.7 V at  $i_C = 1$  mA. Design the circuit so that Collector current is 2 mA and a voltage of +5 V appears at the collector.

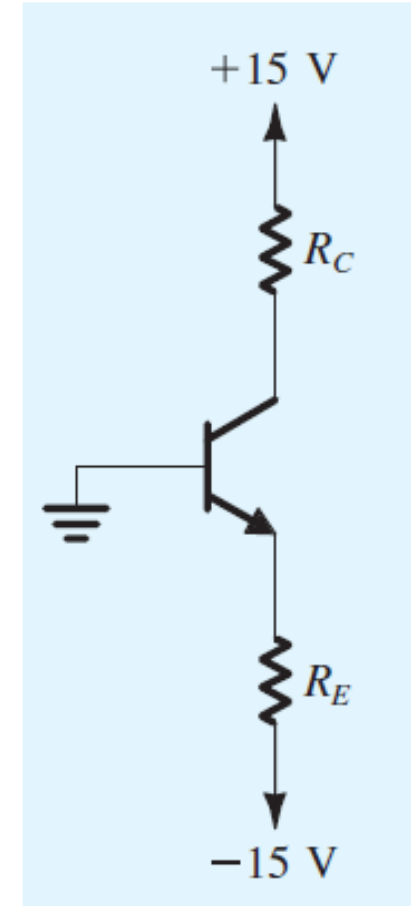- $V_{BE} = 0.717$  V,  $R_C = 5$  K $\Omega$ ,  $R_E = 7.07$  K $\Omega$






For a transistor circuit, the base terminal is grounded, and Collector is connected to a supply voltage of 10 V via  $R_C = 5 \text{ K ohms}$  and emitter is connected to a supply voltage of -10 V via  $R_E = 10 \text{ K ohms}$ , the voltage at the emitter was measured and found to be -0.7 V. if  $\beta = 50$ , find  $I_E$ ,  $I_B$ ,  $I_C$ , and  $V_C$ .

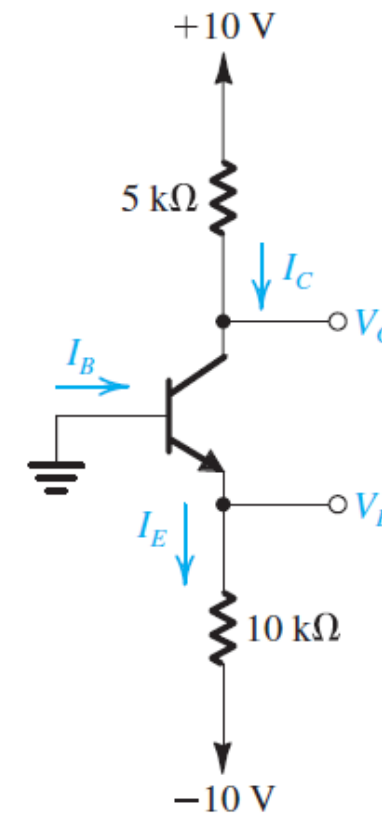- $I_E = 0.93 \text{ mA}$
- $I_B = 18.2 \text{ }\mu\text{A}$
- $I_C = 0.91 \text{ mA}$
- $V_C = 5.45 \text{ V}$






# BJT: operating Configurations

- Symbols and simplified junction models

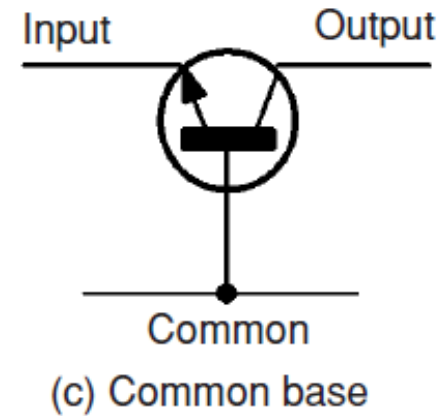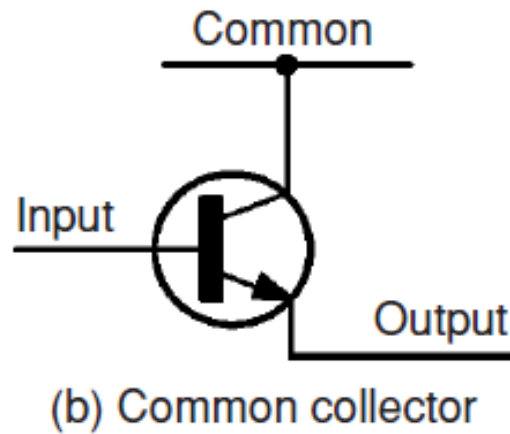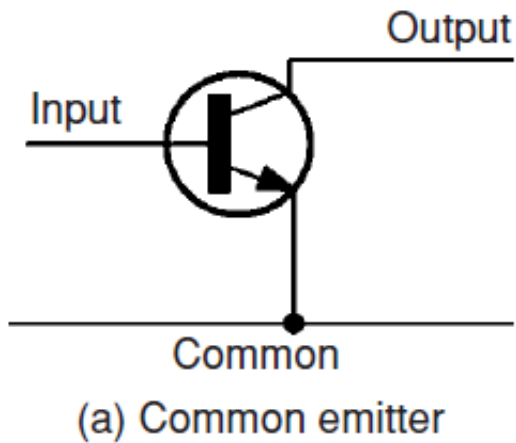




# Common Emitter: Input Characteristics

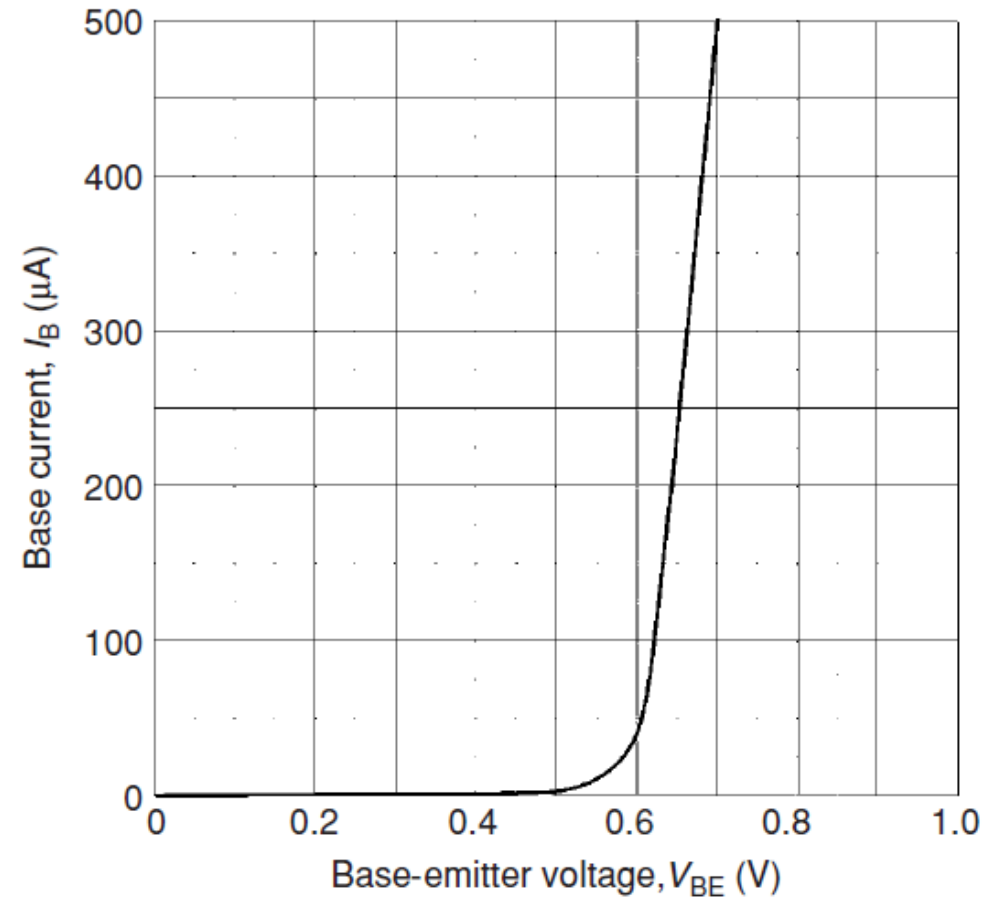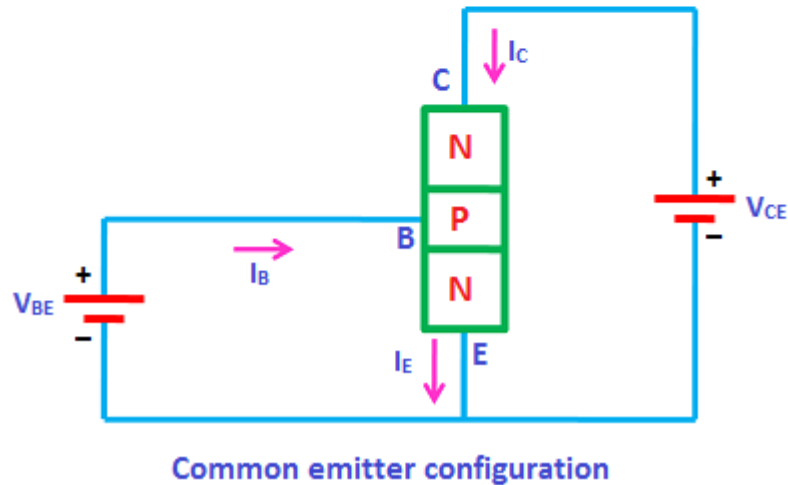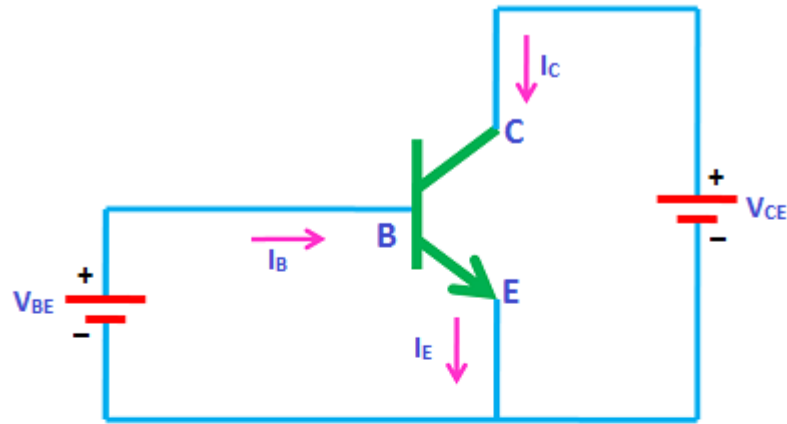

- $V_{BE}$  Vs  $I_B$
- Small current flows until  $V_{BE}$  exceeds 0.6 V, shows the Si diode forward char.
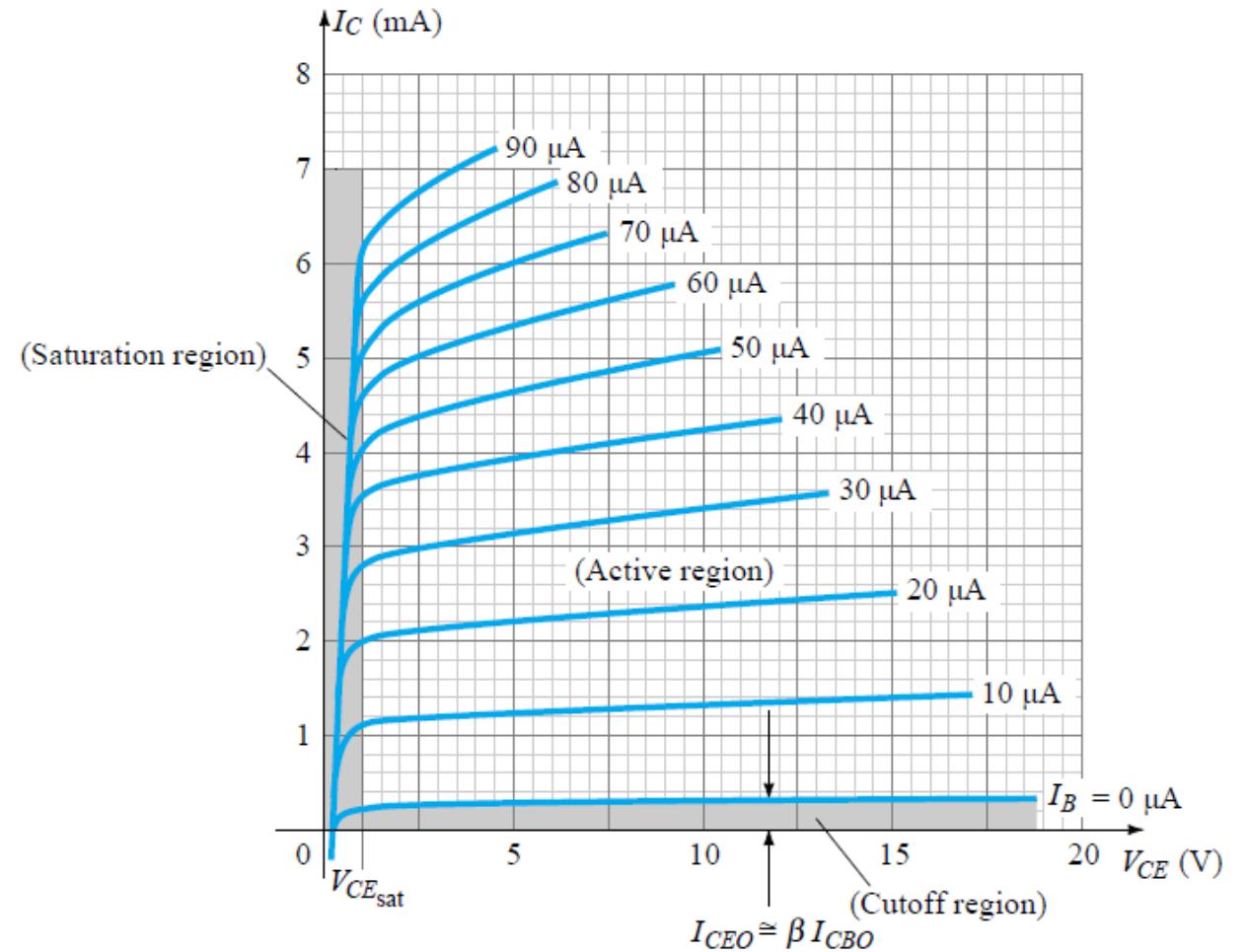
# Common Emitter: Output Characteristics

- $V_{CE}$  Vs  $I_C$
- There modes of operation are shown
- $I_B = 0$  cut-off
- $V_{CE} < V_{CEsat}$  saturation



# BJT: Parameters

- Input resistance:

$$\text{Static (or d.c.) input resistance} = \frac{V_{BE}}{I_B}$$

$$\text{Dynamic (or a.c.) input resistance} = \frac{\Delta V_{BE}}{\Delta I_B}$$

- Output resistance:

$$\text{Static (or d.c.) output resistance} = \frac{V_{CE}}{I_C}$$

$$\text{Dynamic (or a.c.) output resistance} = \frac{\Delta V_{CE}}{\Delta I_C}$$

- Current Gain:


$$\text{Static (or d.c.) current gain} = \frac{I_C}{I_B}$$

$$\text{Dynamic (or a.c.) current gain} = \frac{\Delta I_C}{\Delta I_B}$$


# In Saturation Mode

- Two things need to be verified?
- 1. is the CBJ is forward biased by more than 0.4 V?
- 2. is the ratio if  $i_C/i_B < \beta$


$$\beta_{\text{forced}} = \left. \frac{i_C}{i_B} \right|_{\text{saturation}} \leq \beta$$

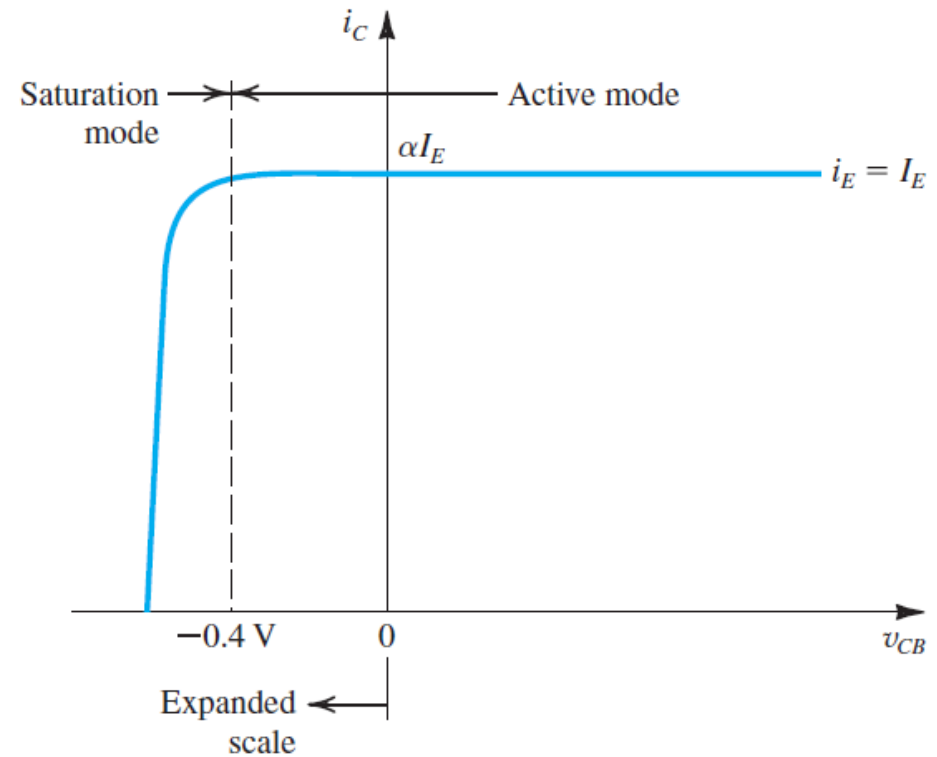
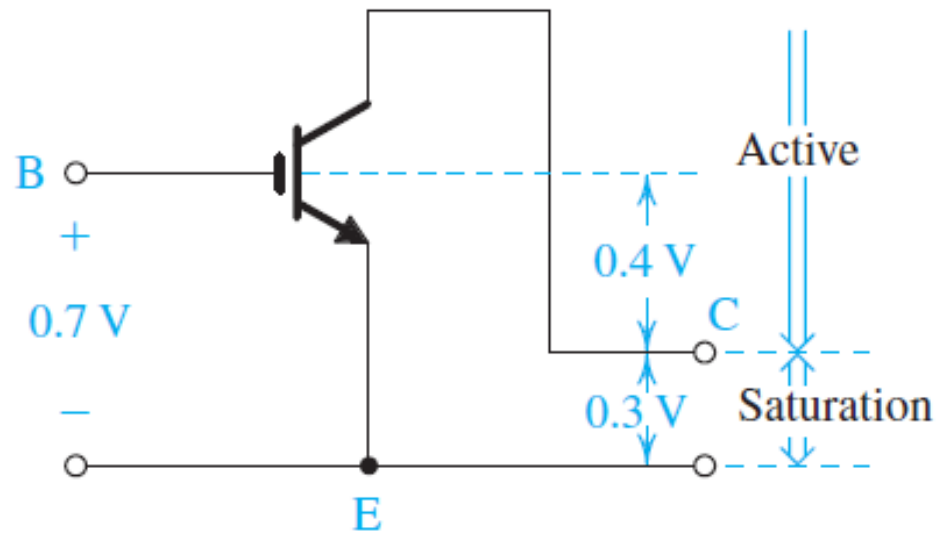
# Condition for operating BJT in active mode and in saturation mode




(a) *nnp*

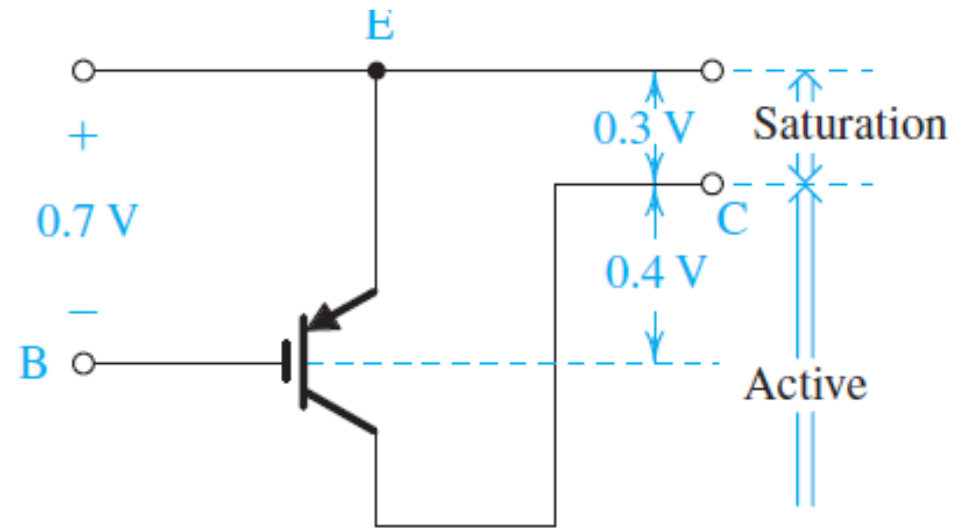

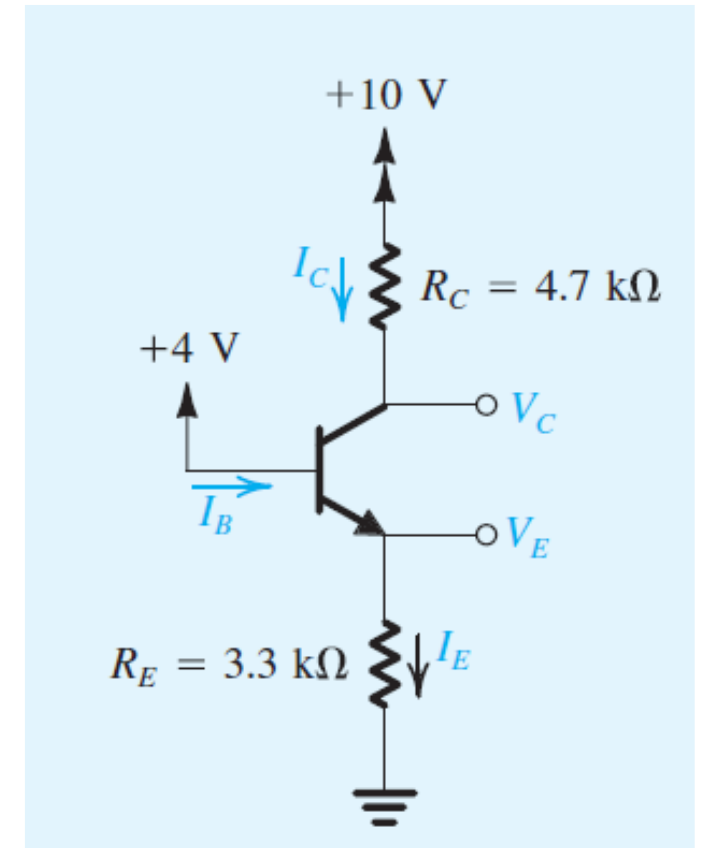(b) *pnp*

Consider the circuit shown in Figure, We wish to analyze this circuit to determine all node voltages and branch currents. We will assume that  $\beta$  is specified to be 100.

- $I_E = 1 \text{ mA}$
- $I_B = 10 \text{ } \mu\text{A}$
- $I_C = 0.99 \text{ mA}$
- $V_C = 5.35 \text{ V}$
- $V_B = 4 \text{ V}$
- $V_E = 3.3 \text{ V}$



We wish to analyze the circuit of Fig. 6.24(a) to determine the voltages at all nodes and the currents through all branches, We will assume that  $\beta$  is specified to be 50.

- $I_E = 1.6 \text{ mA}$
- $I_B = 10 \mu\text{A}$
- $I_C = 0.99 \text{ mA}$
- $V_B = 6 \text{ V}; V_E = 5.3 \text{ V}; V_C = 2.63 \text{ V}$  not in active region
- Then  $V_C = V_E + 0.2 \text{ V} = 5.5 \text{ V}$ ,  $I_C = 0.96 \text{ mA}$
- $\beta_{\text{force}} = i_C / i_B = 0.96 / 0.64 = 1.5$ .

