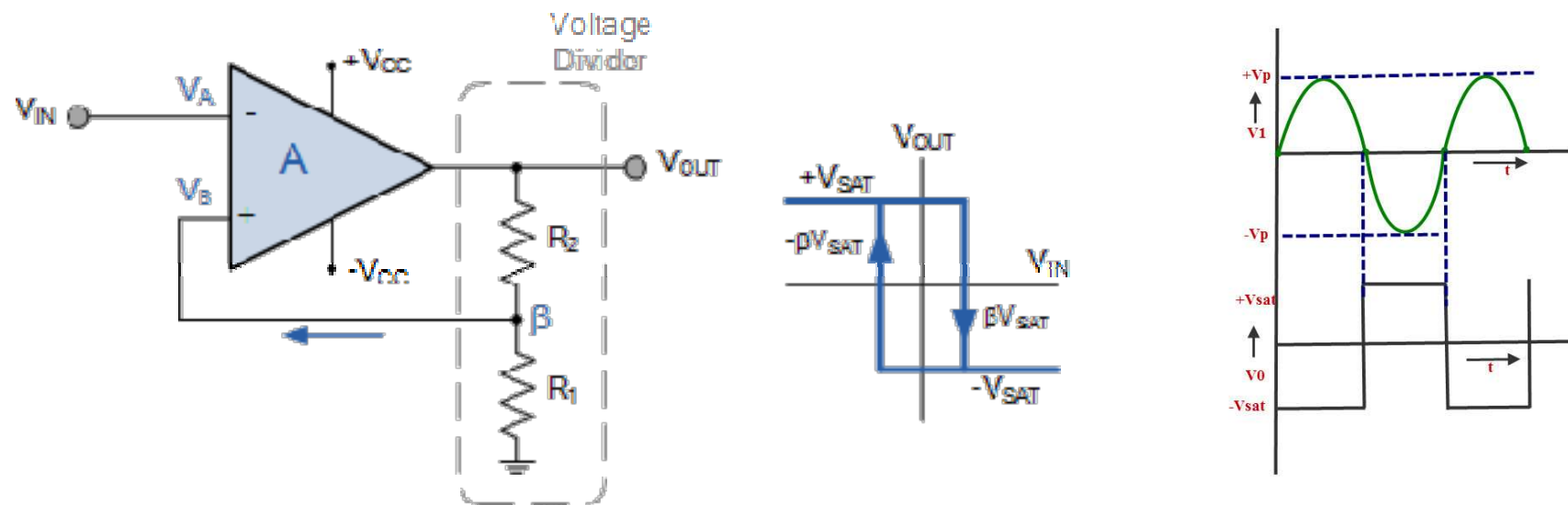


Generation of a Square wave using Astable Multivibrator

- by connecting the bistable multivibrator with an RC circuit in a feedback loop



Square wave Generator

The Square Wave Generator Using Op amp means the astable multivibrator circuit using op-amp, which generates the square wave of required frequency.


It looks like a comparator with hysteresis (schmitt trigger), except that the input voltage is replaced by a capacitor. The circuit has a time dependent elements such as resistance and capacitor to set the frequency of oscillation.

When V_o is at $+V_{sat}$, the feedback voltage is called the upper threshold voltage V_{UT} and is given as

$$V_{UT} = \frac{R_1 \cdot +V_{sat}}{R_1 + R_2}$$


When V_o is at $-V_{sat}$, the feedback voltage is called the lower-threshold voltage V_{LT} and is given as
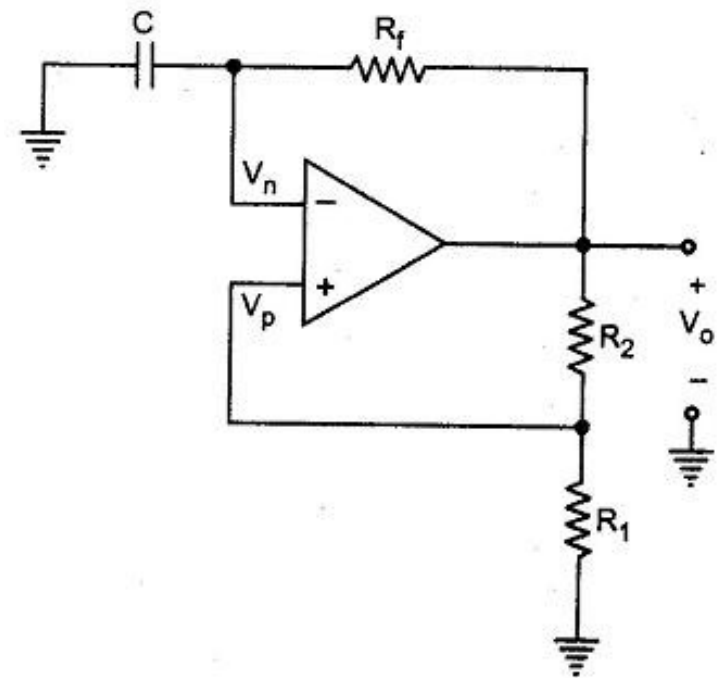
$$V_{LT} = \frac{R_1 \cdot -V_{sat}}{R_1 + R_2}$$




Operation:

- When power is turn ON: V_{out} automatically swings either to $+V_{sat}$ or to $-V_{sat}$ since these are the only stable states allowed by the schmitt trigger.
- Assume it swings to $+V_{sat}$: With $V_o = +V_{sat}$ and $V_p = V_{UT}$ and capacitor starts charging towards $+V_{sat}$ through the feedback path provided by the resistor R_f to the inverting ($-$) input.
- As long as the capacitor voltage V_c is less than V_{UT} , the output voltage remains at $+V_{sat}$.
- As soon as V_c charges to a value slightly greater than V_{UT} , the ($-$) input goes positive with respect to the ($+$) input. This switches the output voltage from $+V_{sat}$ to $-V_{sat}$ and we have $V_p = V_{LT}$ which is negative with respect to ground. As V_o switches to $-V_{sat}$, capacitor starts discharging via R_f .
- The current I – discharges capacitor to 0 V and recharges capacitor to V_{LT} . When V_c becomes slightly more negative than the feedback voltage V_{LT} , output voltage V_o switches back to $+V_{sat}$.

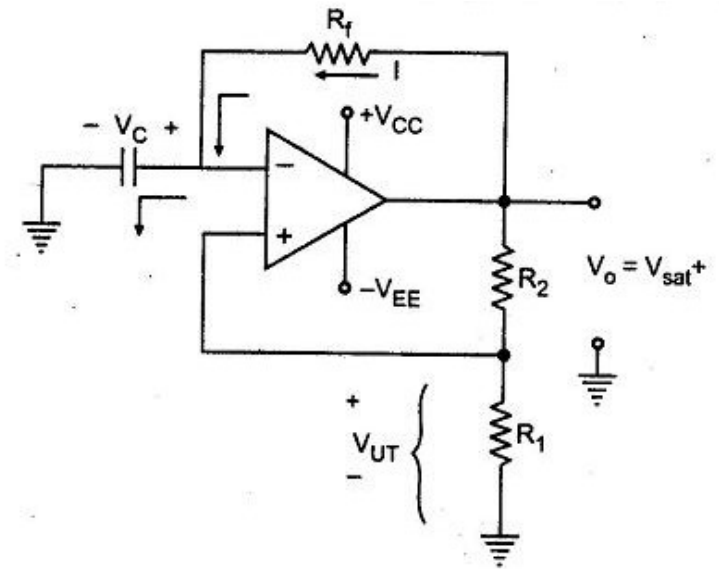

Waveform

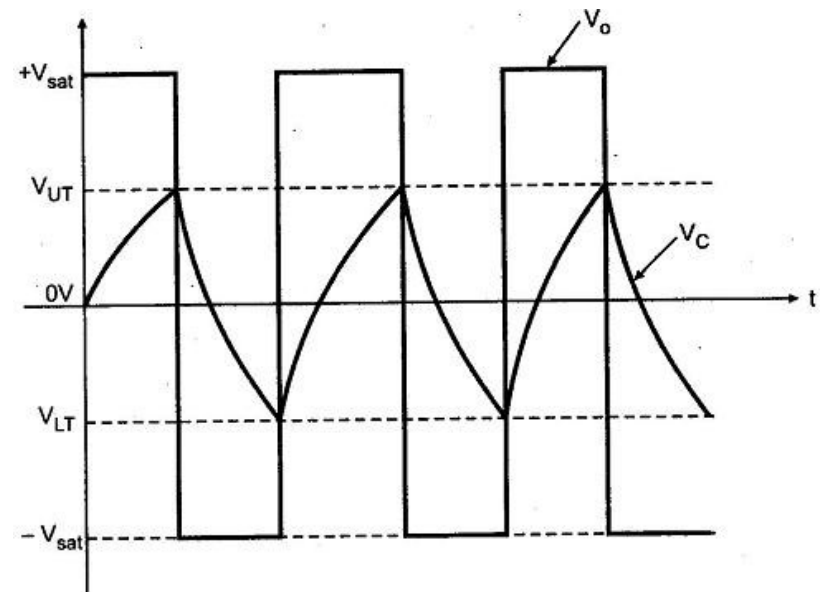- As a result, the condition is reestablished except that capacitor now has a initial charge equal to V_{LT} .
- The capacitor will discharge from V_{LT} to $0V$ and then recharge to V_{UT} , and the process is repeating.
- Once the, initial cycle is completed, the waveforms become periodic.



Frequency of Oscillations

- The frequency of oscillation is determined by the time it takes the [capacitor](#) to charge from V_{LT} to V_{UT} and vice versa. The voltage across the capacitor as a function of time is given as

$$V_C(t) = V_{\max} + (V_{\text{initial}} - V_{\max}) e^{(-t/T)}$$

- where $V_C(t)$ is the instantaneous voltage across the capacitor.
- V_{initial} is the initial voltage
- V_{\max} is the voltage toward which the capacitor is charging.

- Let us consider the charging of capacitor from V_{LT} to V_{UT} , where V_{LT} is the initial voltage, V_{UT} is the instantaneous voltage and $+V_{sat}$ is the maximum voltage. At $t = T_1$, voltage across capacitor reaches V_{UT} and therefore equation becomes

$$V_{UT} = +V_{sat} + (V_{LT} - +V_{sat})e^{(-T_1/R_f C)}$$

$$\therefore -(V_{LT} - +V_{sat})e^{(-T_1/R_f C)} = +V_{sat} - V_{UT}$$

$$\therefore e^{(-T_1/R_f C)} = \frac{(+V_{sat} - V_{UT})}{(+V_{sat} - V_{LT})}$$

$$\frac{-T_1}{R_f C} = \ln \left(\frac{+V_{sat} - V_{UT}}{+V_{sat} - V_{LT}} \right)$$

$$T_1 = -R_f C \ln \left(\frac{+V_{sat} - V_{UT}}{+V_{sat} - V_{LT}} \right)$$

$$= R_f C \ln \left(\frac{+V_{sat} - V_{LT}}{+V_{sat} - V_{UT}} \right)$$

- The time taken by capacitor to charge from V_{UT} to V_{LT} is same as time required for charging capacitor from V_{LT} to V_{UT} . Therefore, total time required for one oscillation is given as

$$T = 2T_1$$

$$= 2R_f C \ln \left(\frac{+V_{sat} - V_{LT}}{+V_{sat} - V_{UT}} \right)$$

$$T = 2R_f C \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$

$$V_{LT} = +\beta V_{sat}$$

$$V_{UT} = +\beta V_{sat}$$

$$\beta = \frac{R_1}{R_1 + R_2}$$


- The frequency of oscillation can be determined as $f_o = 1/T$, where T represents the time required for one oscillation.
- Substituting the value of T we get,

$$f_o = \frac{1}{2R_f C \ln \left(\frac{+V_{sat} - V_{LT}}{+V_{sat} - V_{UT}} \right)}$$

$$f_o = \frac{1}{2R_f C \ln \left(\frac{1 + \beta}{1 - \beta} \right)}$$


Monostable Multivibrator

- At initial power on (that is $t = 0$), the output (V_{OUT}) will saturate towards either the positive rail ($+V_{CC}$), or to the negative rail ($-V_{CC}$), since these are the only two stable states allowed by the op-amp.
- Let's assume for now that the output has swung towards the positive supply rail, $+V_{CC}$. Then the voltage at the non-inverting input, V_B will be equal to $+V_{CC} \cdot \beta$ where β is the feedback fraction.
- The inverting input is held at 0.7 volts, the forward voltage drop of diode, D_1 and clamped to 0V (ground) by the diode, preventing it from going any more positive. Thus the potential at V_A is much less than that at V_B and the output remains stable at $+V_{CC}$.
- At the same time, the capacitor, (C) charges up to the same 0.7 volts potential and is held there by the forward-biased voltage drop of the diode.

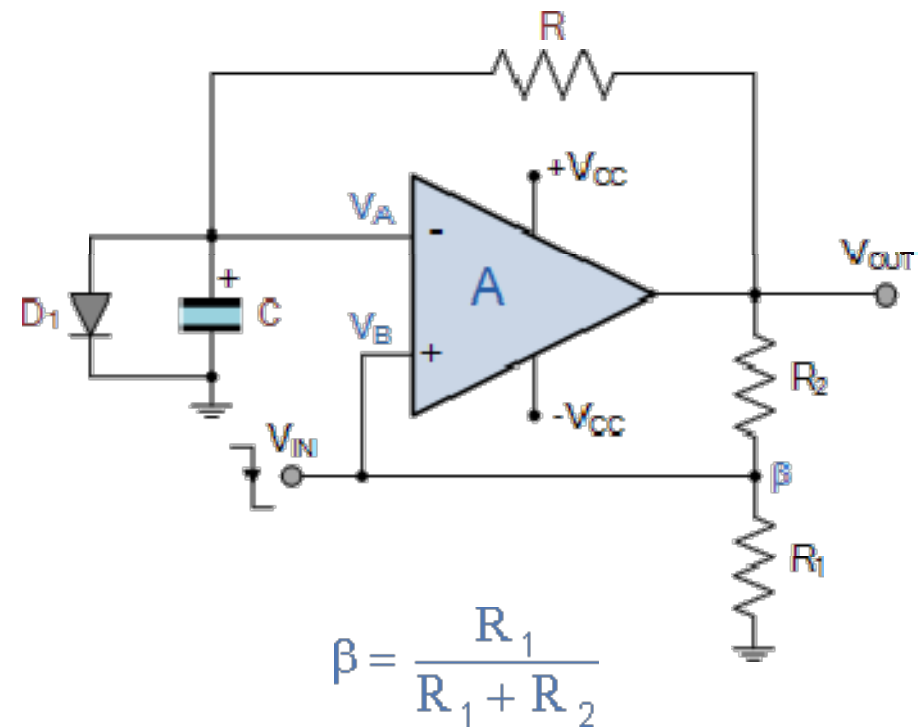


Monostable Multivibrator

- If we were to apply a negative pulse to the non-inverting input, the 0.7v voltage at V_A now becomes greater than the voltage at V_B since V_B is now negative. Thus the output of the Schmitt configured op-amp switches state and saturates towards the negative supply rail, $-V_{CC}$. The result is that the potential at V_B is now equal to $-V_{CC} \cdot \beta$.
- This temporary meta-stable state causes the capacitor to charge up exponentially in the opposite direction through the feedback resistor, R from +0.7 volts down to the saturated output which it has just switched too, $-V_{CC}$. Diode, D_1 becomes reverse-biased so has no effect. The capacitor, C will discharge at a time constant $\tau = RC$.
- As soon as the capacitor voltage at V_A reaches the same potential as V_B , that is $-V_{CC} \cdot \beta$, the op-amp switches back to its original permanent stable state with the output saturated once again at $+V_{CC}$.

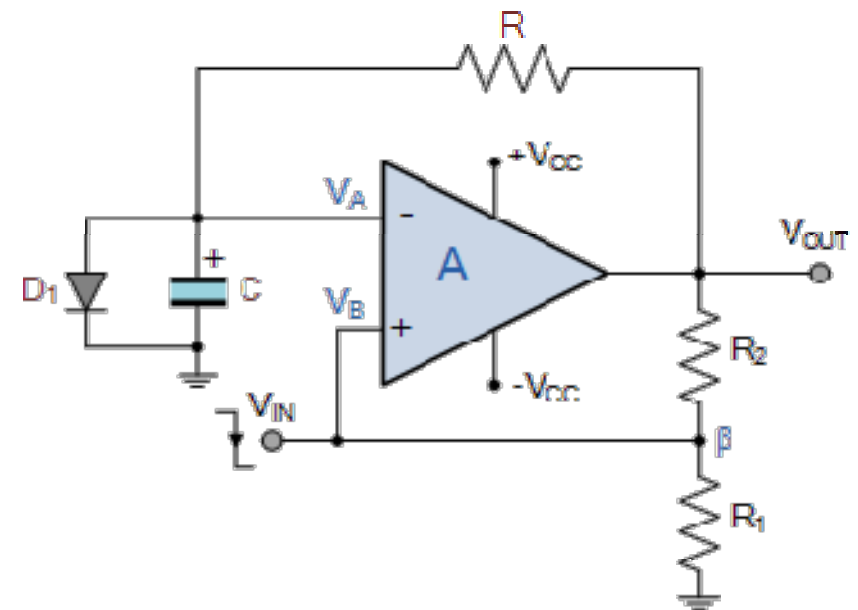


Waveform

- Note that once the timing period is complete and the op-amps output changes back to its stable state and saturates towards the positive supply rail, the capacitor tries to charge up in reverse to $+V_{CC}$ but can only charge to a maximum value of $0.7V$ given by the diodes forward voltage drop. We can show this effect graphically as:
- Then we can see that a negative-going trigger input, will switch the op-amp monostable circuit into its temporary unstable state. After a time delay, T while the capacitor, C charges up through the feedback resistor, R , the circuit switches back to its normal stable state once the capacitor voltage reaches the required potential.

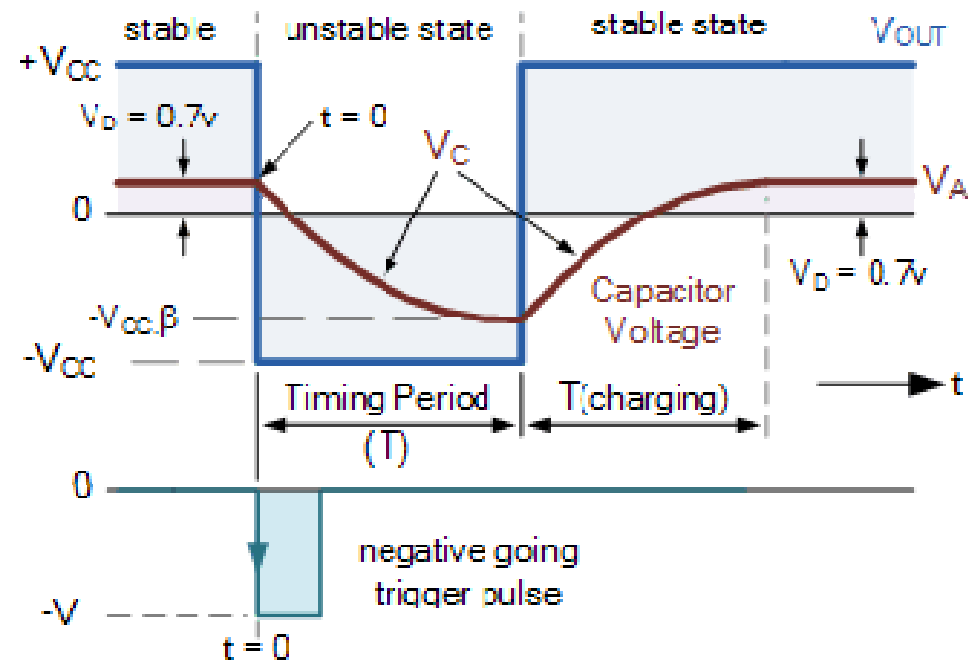

With RC differentiator circuit

- The advantage of using a differentiator circuit is that any constant DC voltage or slowly varying signal will be blocked allowing only rapidly varying trigger pulses to initiate the monostable timing period. Diode, D ensures that the trigger pulse arriving at the op-amps non-inverting input is always negative.
- Generally for a RC differentiator circuit, the peak value of the negative spike is approximately equal to the magnitude of the trigger waveform. Also, as a general rule-of-thumb, for an RC differentiator circuit to produce good sharp narrow spikes, the time constant, (τ) should be at least ten times smaller than the input pulse width.

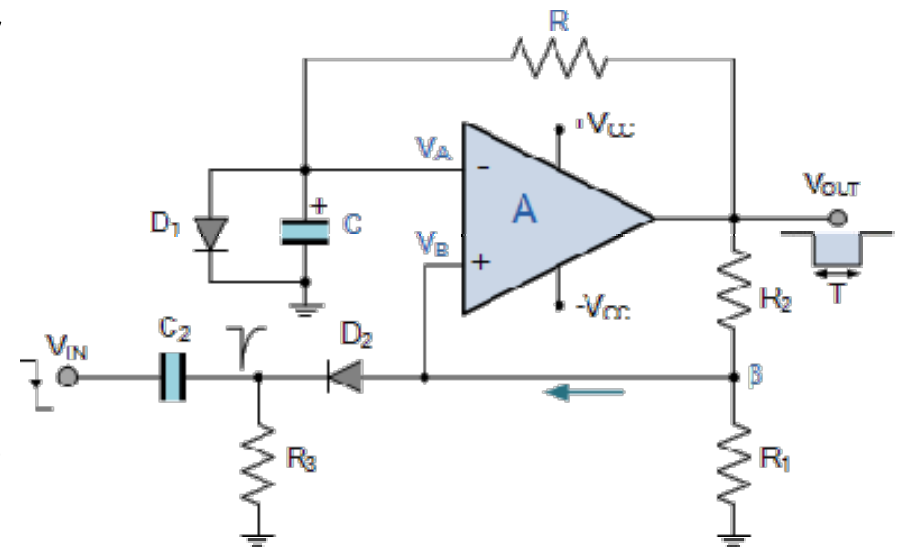


Time Period

- Solution for single time constant RC circuit, $v_o = V_f + (V_i - V_f)e^{-t/RC}$
- For the circuit, $V_f = -V_{sat}$, and $V_i = V_D$; $v_c = -V_{sat} + (V_D + V_{sat})e^{-t/RC}$
- At $t = T$ $v_c = -\beta V_{sat}$ then $-\beta V_{sat} = -V_{sat} + (V_D + V_{sat})e^{-T/RC}$
- Pulse width T
$$T = RC \ln \frac{(1 + V_D/V_{sat})}{1 - \beta}$$
- If, $V_{sat} \gg V_D$ $R_1 = R_2$ so that $\beta = 0.5$, $T = 0.69RC$

555 Timer

- The circuit consists of two comparators, an SR flip-flop, and a transistor $Q1$ that operates as a switch. One power supply (V_{CC}) is required for operation.
- A resistive voltage divider, consisting of the three equal-valued resistors labeled R_1 , is connected across V_{CC} and establishes the reference (threshold) voltages for the two comparators. These are $V_{TH} = 2/3 V_{CC}$ for comparator 1 and $V_{TL} = 1/3 V_{CC}$ for comparator 2.

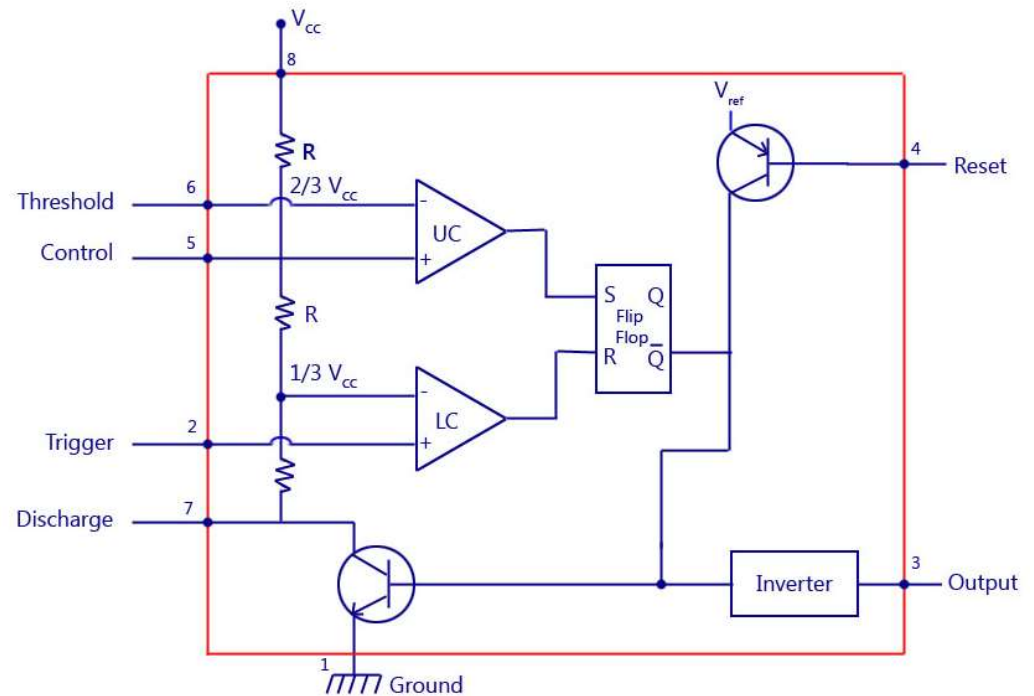

- Here note that an SR flip-flop is a bistable circuit having complementary outputs, denoted Q and \bar{Q} . In the *set* state, the output at Q is “high” (approximately equal to V_{CC}) and that at \bar{Q} is “low” (approximately equal to 0 V).
- In the other stable state, termed the *reset* state, the output at Q is low and that at \bar{Q} is high. The flip-flop is set by applying a high level (V_{CC}) to its set input terminal, labeled S . To reset the flip-flop, a high level is applied to the reset input terminal, labeled R . Note that the reset and set input terminals of the flip-flop in the 555 circuit are connected to the outputs of comparator 1 and comparator 2, respectively.
- The positive-input terminal of comparator 1 is brought out to an external terminal of the 555 package, labeled Threshold. Similarly, the negative-input terminal of comparator 2 is connected to an external terminal labeled Trigger, and the collector of transistor $Q1$ is connected to a terminal labeled Discharge.