



Indian Institute of Information Technology, Sri City, Chittoor
(An Institute of National Importance under an Act of Parliament)

Op-Amp as Integrator and Differentiator

Dr. Kandimalla Divyabramham


Assistant Professor

IIIT Sri City

The Inverting Integrator

$$v_C(t) = V_C + \frac{1}{C} \int_0^t i_1(t) dt$$
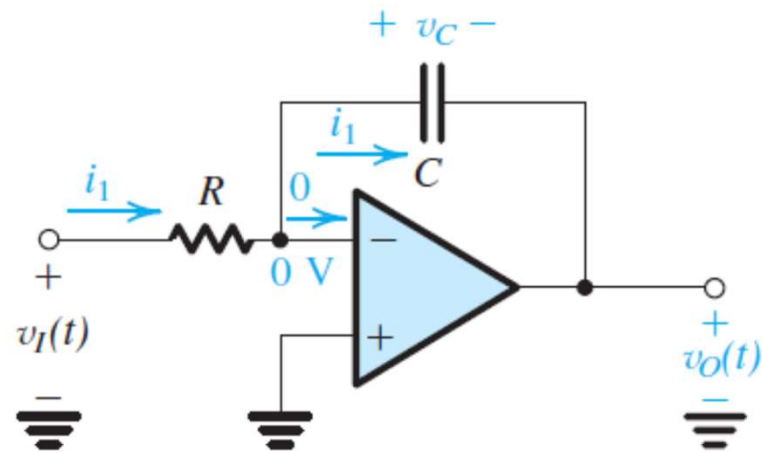
$$v_O(t) = -\frac{1}{CR} \int_0^t v_I(t) dt - V_C$$



$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{1}{j\omega CR}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\omega CR}$$


Example:

- Use an ideal op-amp to design an inverting integrator with an input resistance of $10\text{ k}\Omega$ and an integration time constant of 10^{-3} s . What is the gain magnitude and phase angle of this circuit at 10 rad/s and at 1 rad/s ? What is the frequency at which the gain magnitude is unity?

Circuit with finite gain at DC


$$V_o = -\frac{1}{j\omega RC + R/R_F} V_i$$

$$\left| \frac{V_o}{V_i} \right| = \frac{R_F/R}{\sqrt{1 + (\omega R_F C)^2}}$$

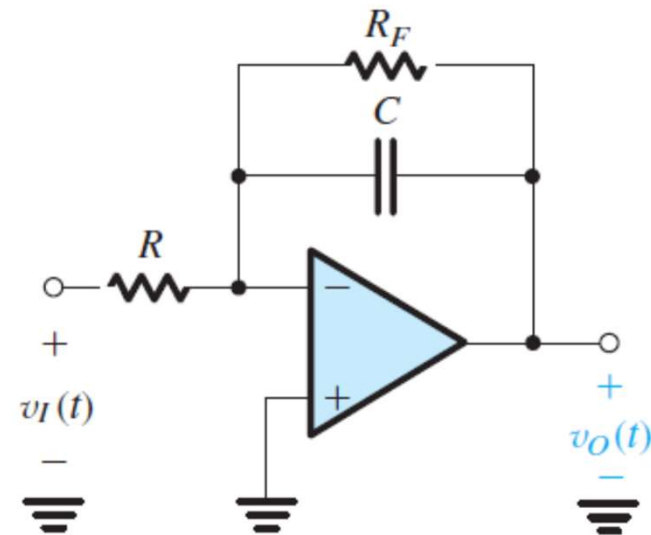

Differentiator Circuit

$$V_o = -j\omega RC_F V_i$$

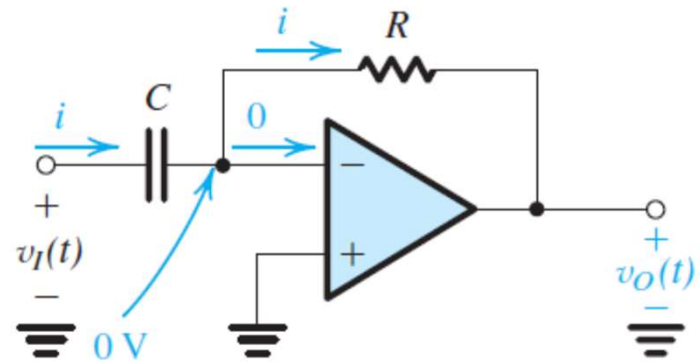

Example:

- Design a differentiator to have a time constant of 10^{-2} s and an input capacitance of $0.01 \mu\text{F}$. What is the gain magnitude and phase of this circuit at 10 rad/s , and at 10^3 rad/s ? In order to limit the high-frequency gain of the differentiator circuit to 100, a resistor is added in series with the capacitor. Find the required resistor value.