



**Indian Institute of Information Technology, Sri City, Chittoor**  
(An Institute of National Importance under an Act of Parliament)

# Analog to Digital and Digital to Analog Converters

Dr. Kandimalla Divyabramham

Assistant Professor

IIIT Sri City

# Contents

---



- Digital to Analog Converters
  - Introduction
  - Usng Binary-weighted resistor
  - R-2R ladder network
- Analog to Digital Converters
  - Introduction
  - Flash ADC
  - Successive Approximations ADC
  - Counting ADC

# Introduction

---

- Physical quantities (e.g., Temperature, a voltage or a speech signal) are analog in nature, varying continuously with time.
- Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.
- An ADC (Analog-to-Digital Converter) is used to convert an analog signal to the digital format.
- The reverse conversion (from digital to analog) is also required. For example, music stored in a DVD in digital format must be converted to an analog voltage for playing out on a speaker.
- A DAC (Digital-to-Analog Converter) is used to convert a digital signal to the analog format.


# Digital to Analog Converters

 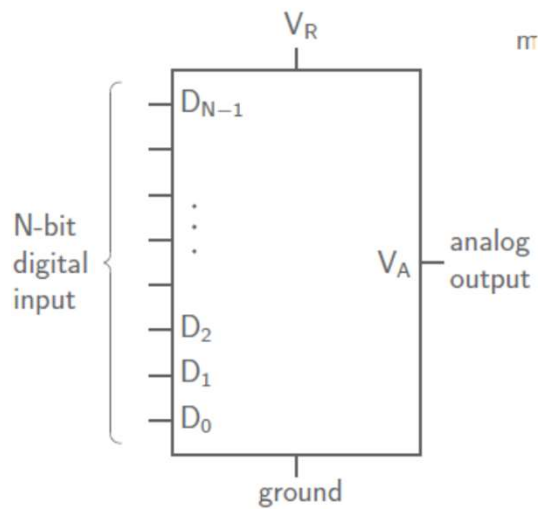

For a 4-bit DAC, with input  $S_3 S_2 S_1 S_0$ , the output voltage is  $V_A = K [(S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0)]$ .  
In general,  $V_A = K \sum_{k=0}^{N-1} S_k 2^k$ .

$K$  is proportional to the reference voltage  $V_R$ . Its value depends on how the DAC is implemented.

# DAC using Binary-weighted resistors

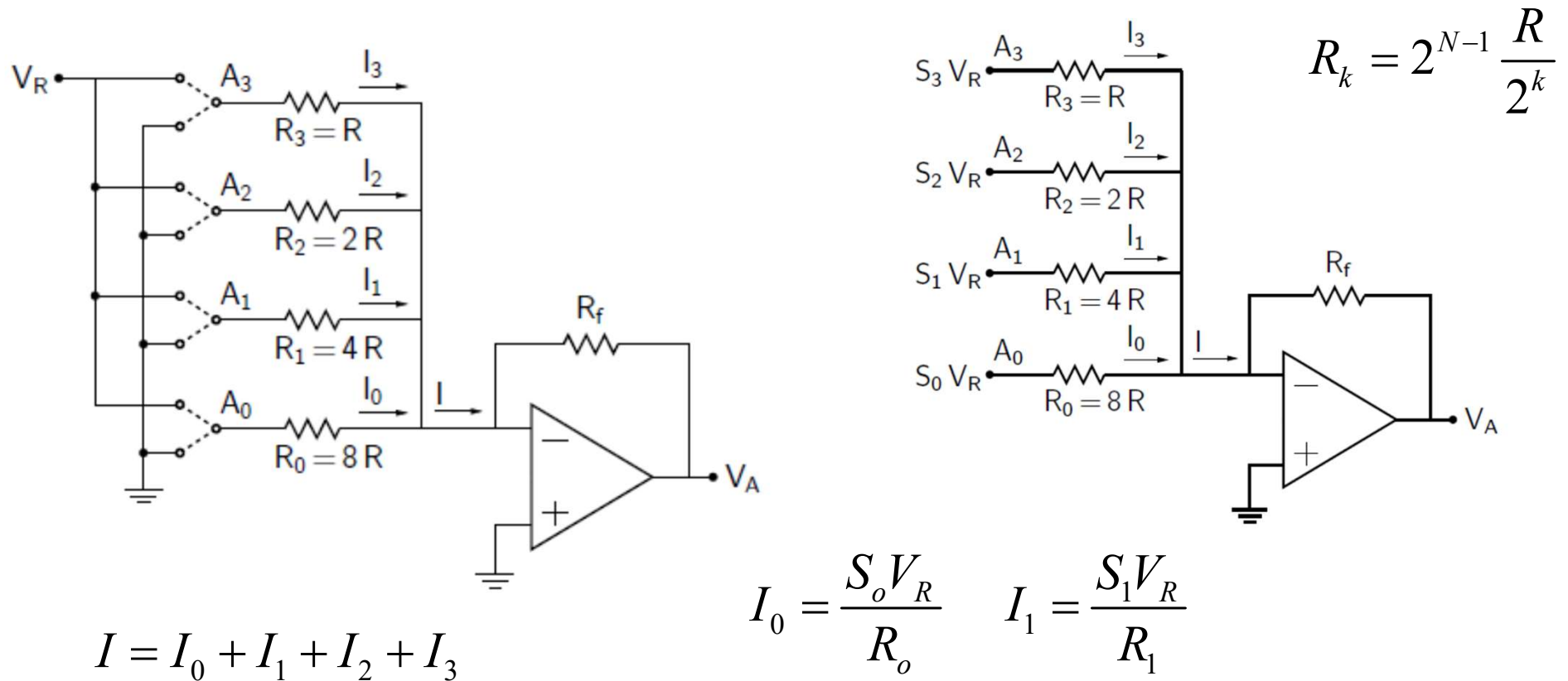

# DAC using Binary-weighted resistors

If the input bit  $S_k$  is 1,  $A_k$  gets connected to  $V_R$ ; else, it gets connected to ground.

$$\rightarrow V(A_k) = S_k \times V_R.$$

Since the inverting terminal of the Op Amp is at virtual ground,

$$I_k = \frac{V(A_k) - 0}{R_k} = \frac{S_k V_R}{R_k}.$$

Using  $R_k = 2^{N-1} R / 2^k$ , we get  $I = \frac{V_R}{2^{N-1} R} \sum_0^{N-1} S_k \times 2^k$  ( $N = 4$  here).

The output voltage is  $V_o = -R_f I = -V_R \frac{R_f}{2^{N-1} R} \sum_0^{N-1} S_k \times 2^k$ .

- Consider an 8-bit DAC with  $V_R = 5$  V. What is the smallest value of  $R$  which will limit the current drawn from the supply ( $V_R$ ) to 10 mA?


Maximum current is drawn from  $V_R$  when the input is 1111 1111.

→ All nodes  $A_0$  to  $A_7$  get connected to  $V_R$ .

$$\rightarrow 10 \text{ mA} = \frac{V_R}{R} + \frac{V_R}{2R} + \dots + \frac{V_R}{2^7 R} = \frac{1}{2^7} \frac{V_R}{R} (2^0 + 2^1 + \dots + 2^7)$$

$$= \frac{1}{2^7} \frac{V_R}{R} (2^8 - 1) = \frac{255}{128} \frac{V_R}{R}$$

 
$$\rightarrow R_{\min} = \frac{5 \text{ V}}{10 \text{ mA}} \times \frac{255}{128} = 996 \Omega .$$



- If  $R_f = R$ , what is the resolution (i.e.,  $V_A$  corresponding to the input LSB changing from 0 to 1 with other input bits constant)?

$$V_A = -V_R \frac{R_f}{2^{N-1}R} [S_7 2^7 + \dots + S_1 2^1 + S_0 2^0]$$
 
$$\rightarrow \Delta V_A = \frac{V_R}{2^{N-1}} \frac{R_f}{R} = \frac{5 \text{ V}}{2^{8-1}} \times 1 = \frac{5}{128} = 0.0391 \text{ V}.$$



- What is the maximum output voltage (in magnitude)?

$$V_A = -\frac{V_R}{2^{N-1}} \frac{R_f}{R} [S_7 2^7 + \dots + S_1 2^1 + S_0 2^0].$$

Maximum  $V_A$  (in magnitude) is obtained when the input is 1111 1111.


$$|V_A|^{\max} = \frac{5}{128} \times 1 \times [2^0 + 2^1 + \dots + 2^7] = \frac{5}{128} \times (2^8 - 1) = 5 \times \frac{255}{128} = 9.961 \text{ V}.$$



- Find the output voltage corresponding to the input 1010 1101.



$$\begin{aligned} V_A &= -\frac{V_R}{2^{N-1}} \frac{R_f}{R} \left[ S_7 2^7 + \dots + S_1 2^1 + S_0 2^0 \right] . \\ &= -\frac{5}{128} \times 1 \times \left[ 2^7 + 2^5 + 2^3 + 2^2 + 2^0 \right] = -5 \times \frac{173}{128} = -6.758 \text{ V} . \end{aligned}$$

# DAC with R-2R Ladder

 


Node  $A_k$  is connected to  $V_R$  if input bit  $S_k$  is 1; else, it is connected to ground.



The original network is equivalent to

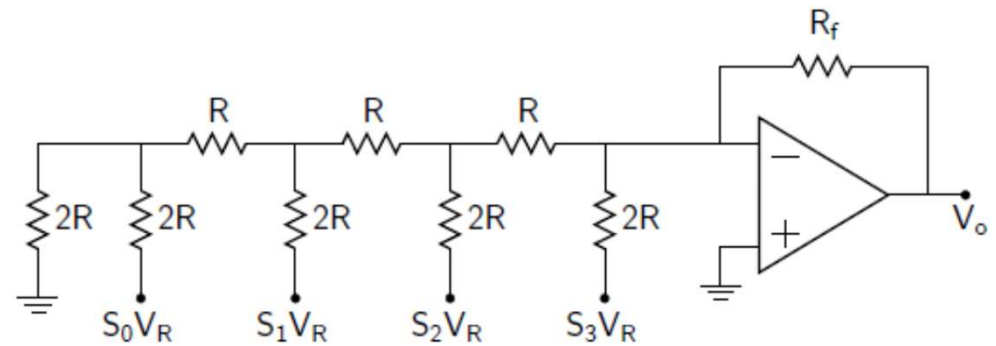 



# R-2R Ladder Network

 

 
 
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$



  
# R-2R ladder network: $V_{Th}$ for $S_1 = 1$



  
# R-2R ladder network: $V_{Th}$ for $S_2 = 1$


 
# R-2R ladder network: $V_{Th}$ for $S_3 = 1$



 


$$R_{Th} = R.$$

$$V_{Th} = V_{Th}^{(S_0)} + V_{Th}^{(S_1)} + V_{Th}^{(S_2)} + V_{Th}^{(S_3)}$$

$$= \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3].$$

 We can use the  $R$ - $2R$  ladder network and an Op Amp



$$V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3].$$

$$\text{For an } N\text{-bit DAC, } V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_{k=0}^{N-1} S_k 2^k.$$

6- to 20-bit DACs based on the  $R$ - $2R$  ladder network are commercially available in monolithic form (single chip).