



Indian Institute of Information Technology, Sri City, Chittoor
(An Institute of National Importance under an Act of Parliament)

BEC Tutorial 3


Dr. Kandimalla Divyabramham
Assistant Professor
IIIT Sri City

Rectifier problem

- A full-wave bridge-rectifier circuit with a 1-k load operates from a 120-V (rms) 60-Hz household supply through a 12-to-1 step-down transformer having a single secondary winding. It uses four diodes, each of which can be modeled to have a 0.7-V drop for any current. What is the peak value of the rectified voltage across the load? For what fraction of a cycle does each diode conduct? What is the average voltage across the load? What is the average current through the load?

Transistor

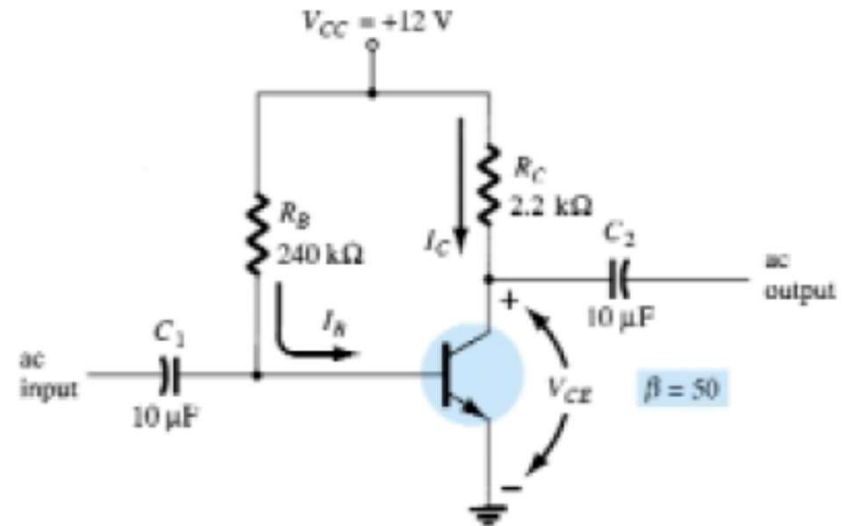- Determine the following for the fixed-bias configuration .
- (a) I_B and I_C .
- (b) V_{CE} .
- (c) V_B and V_C .
- (d) V_{BC} .



Transistor

- For the circuit shown here, find V_B , V_E , and V_C
- for $R_B = 100\text{ k}$, 10 k , and 1 k . Let $\beta=100$.

