



Indian Institute of Information Technology, Sri City, Chittoor
(An Institute of National Importance under an Act of Parliament)

BEC Tutorial 7


Dr. Kandimalla Divyabramham

Assistant Professor

IIIT Sri City

Differentiator

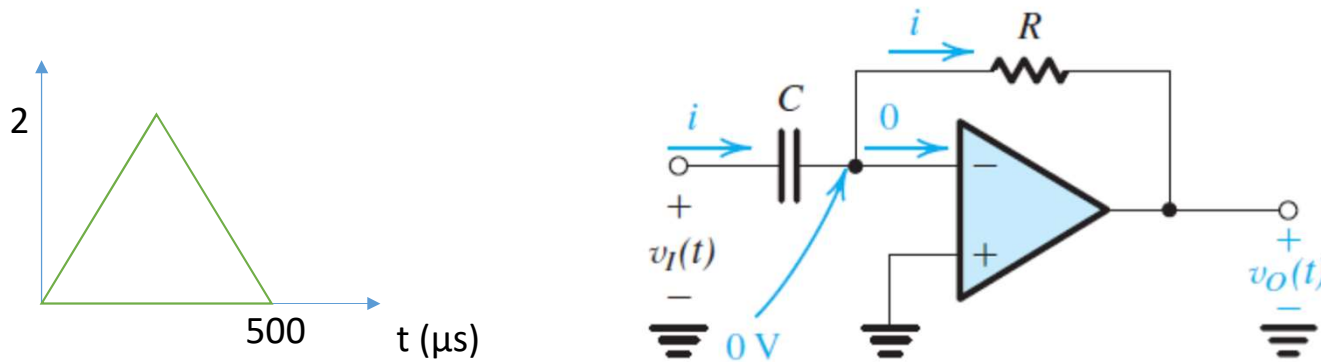- Input of the Differentiator is given as, find output if $R_F = 2 \text{ k}\Omega$, and $C_1 = 0.1 \text{ }\mu\text{F}$.



Wien bridge oscillator

- A wien bridge oscillator is having $R_f = 6.4 \text{ K}\Omega$, $R_i = 3.2 \text{ K}\Omega$, series combination ($R_1 = 5 \text{ K}\Omega$, $C_1 = 7.5 \text{ nF}$), and parallel combination ($R_2 = 13 \text{ K}\Omega$ and $C_2 = 4.65 \text{ nF}$). Determine the transfer function of the feed back network (V_a/V_o), also determine the frequency of oscillations.


$$Z_p = \frac{1}{Y_p} = \frac{1}{\frac{1}{R_2} + j\omega C_2} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$Z_s = \frac{1}{j\omega C_1} + R_1 = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$Z_s + Z_p = \frac{1 + j\omega R_1 C_1}{j\omega C_1} + \frac{R_2}{1 + j\omega R_2 C_2} = \frac{1 - \omega^2 R_1 C_1 R_2 C_2 + j\omega(R_1 C_1 + R_2 C_2 + R_2 C_1)}{j\omega C_1 (1 + j\omega R_2 C_2)}$$

$$\beta = \frac{Z_p}{Z_p + Z_s} = \frac{j\omega R_2 C_1}{1 - \omega^2 R_1 C_1 R_2 C_2 + j\omega(R_1 C_1 + R_2 C_2 + R_2 C_1)}$$
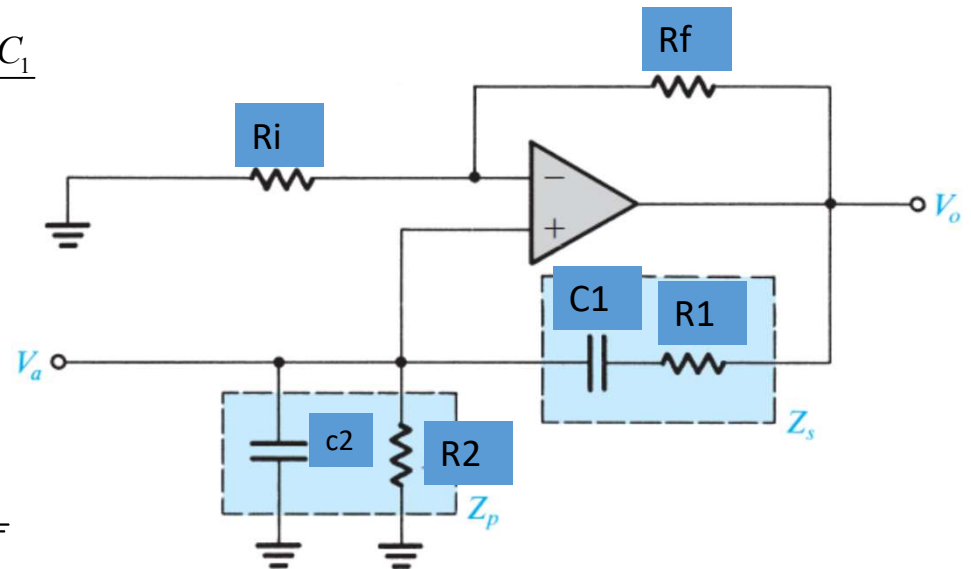
$$1 - \omega^2 R_1 C_1 R_2 C_2 = 0 \quad f = \frac{1}{2\pi \sqrt{R_1 C_1 R_2 C_2}}$$



Schmitt Trigger

An operational amplifier is to be used with positive feedback to produce a Schmitt trigger circuit. If resistor, $R_1 = 90\text{k}\Omega$ and resistor, $R_2 = 10\text{k}\Omega$, what will be the values of the upper and lower switching points of the reference voltage and the width of the hysteresis if the op-amp is connected to a dual $\pm 10\text{V}$ power supply. (i) $V_{ref} = 0\text{ V}$ and (ii) $V_{ref} = 4\text{ V}$.

$$V_{UT} = \frac{R_1}{R_1 + R_2} V_{ref} + \frac{R_2}{R_1 + R_2} V_{sat}$$

$$V_{LT} = \frac{R_1}{R_1 + R_2} V_{ref} - \frac{R_2}{R_1 + R_2} V_{sat}$$

$$V_H = \frac{2R_2}{R_1 + R_2} V_{sat}$$

