
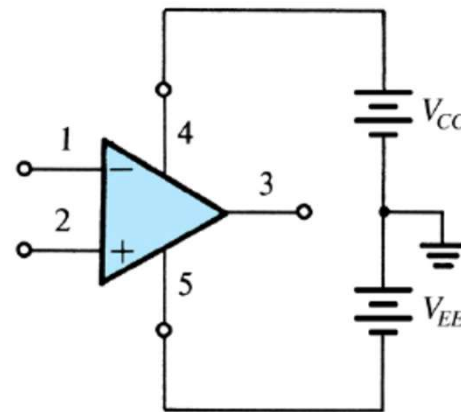
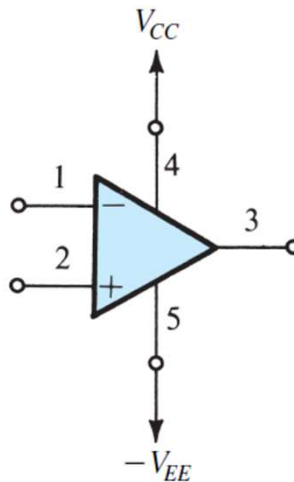


BASIC ELECTRONIC CIRCUITS


Amplifiers, and Op-Amps

The Ideal Op-Amp: terminals

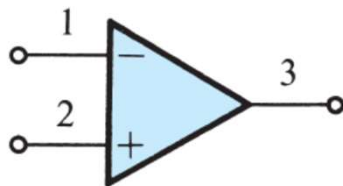- 3 terminals: Two input and one output.
- No terminal of the op-amp package is physically connected to ground.




Pin configuration

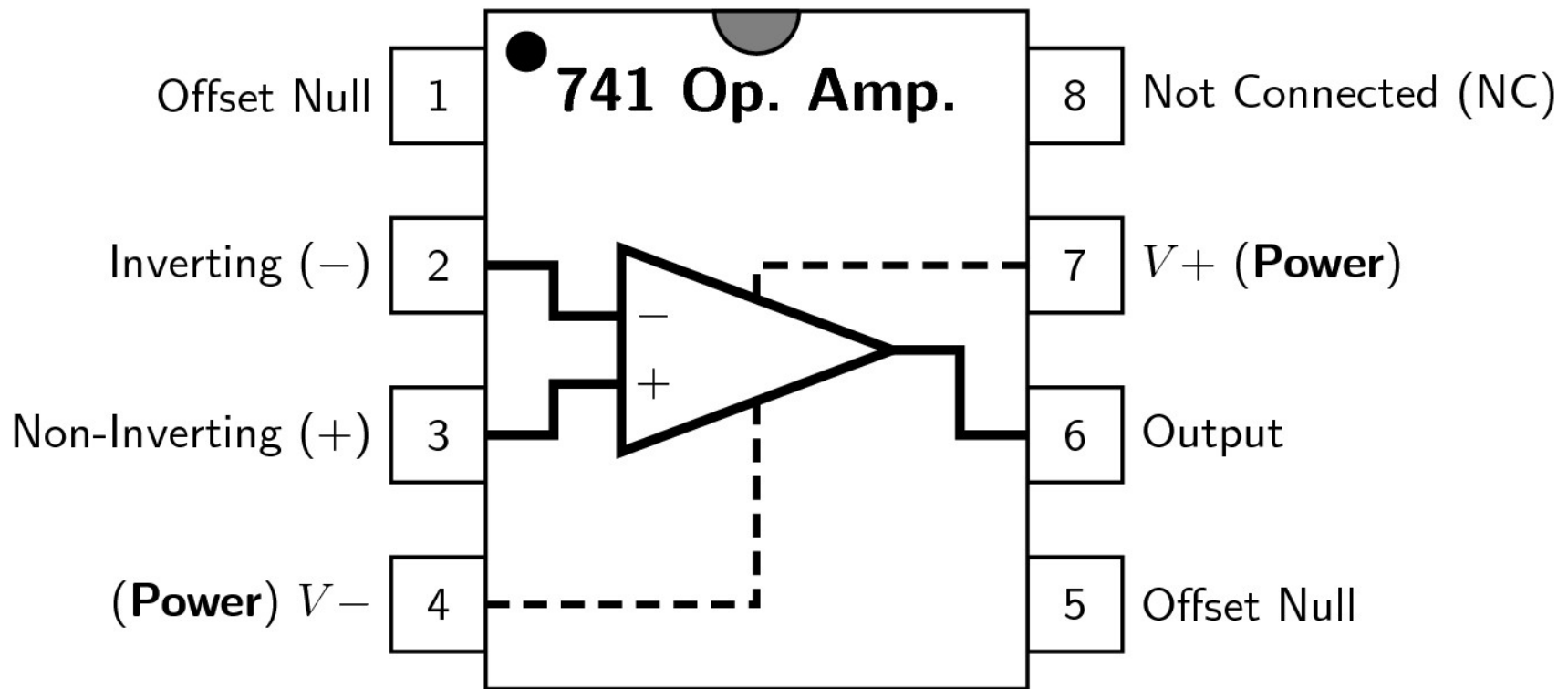

Function and characteristics

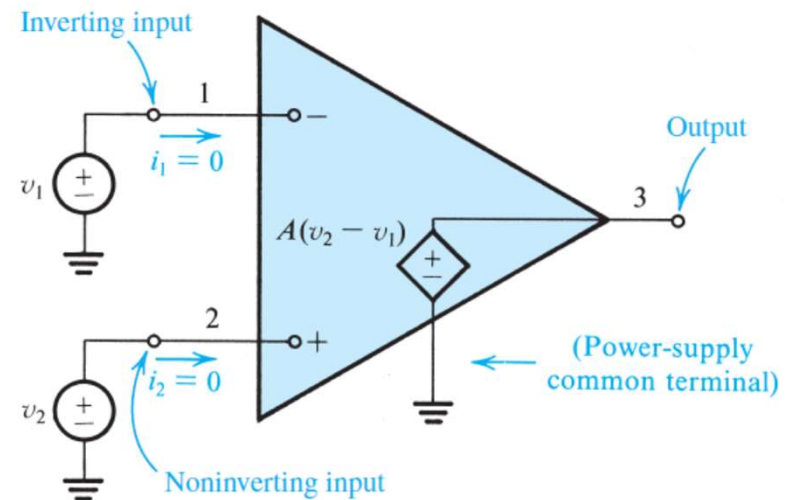
- Basic function is to sense the difference between the voltage signals applied at its input terminals.
 - Infinite input impedance
 - Zero output impedance
 - Zero common mode gain
 - Infinite open-loop gain A
 - Infinite bandwidth




Equivalent Circuit (VCVS) model of the ideal OP-AMP

Differential input, single-ended output amplifier


Inverting Configuration

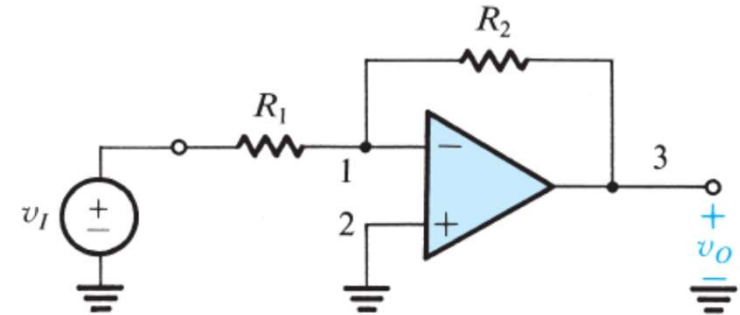

"negative feedback"

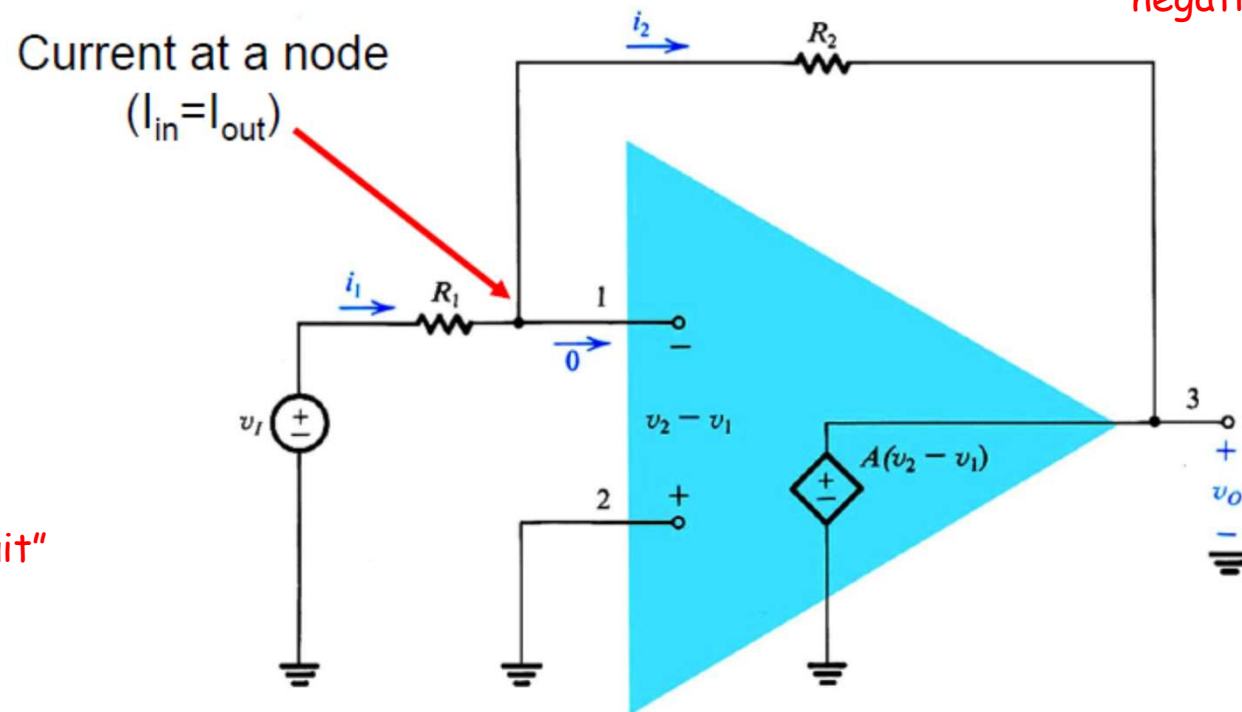

"Virtual short Circuit"

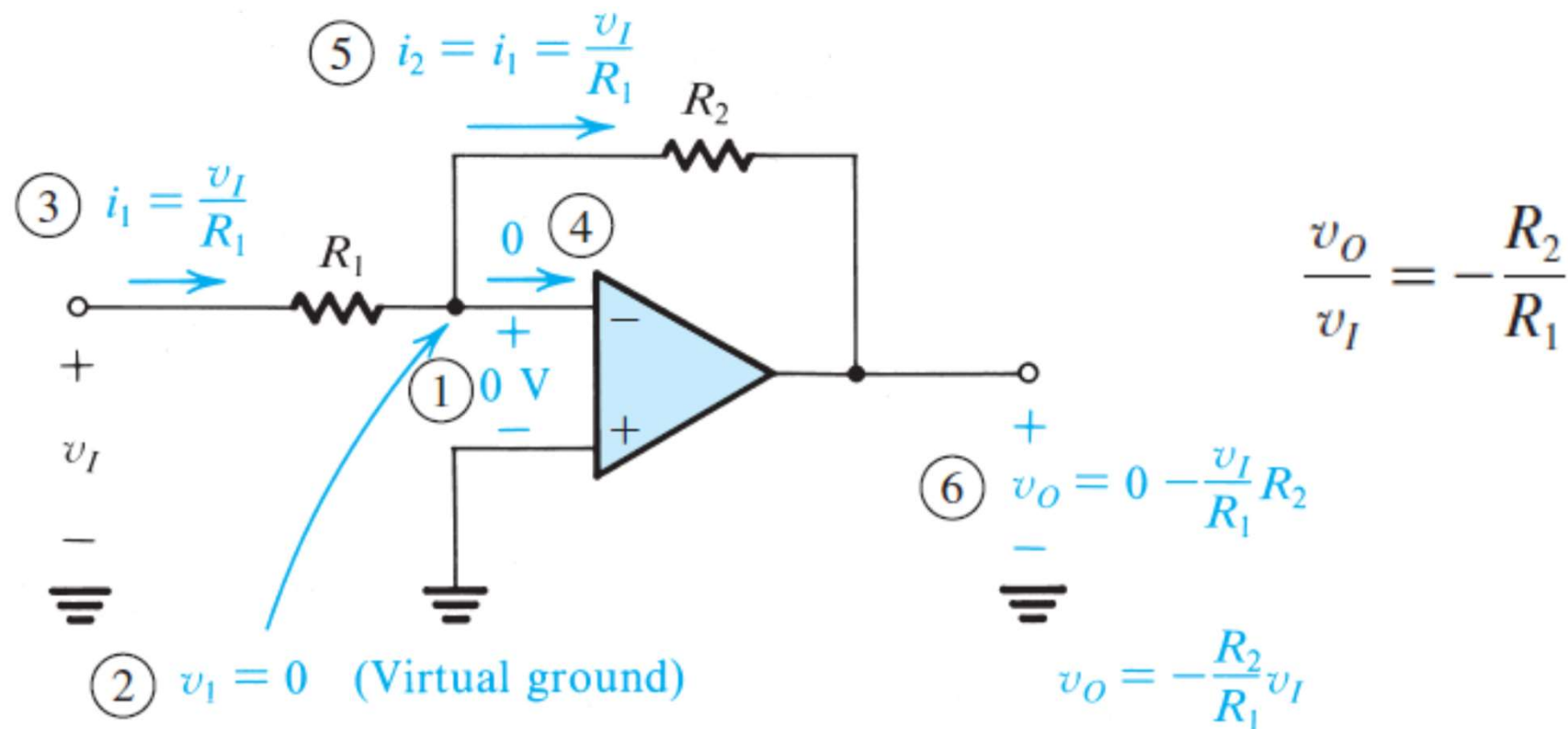


Closed loop gain is independent of open-loop gain, entirely depends on the passive elements.

Application: The weighted Summer


$$i = i_1 + i_2 + \cdots + i_n$$

$$v_O = 0 - iR_f = -iR_f$$

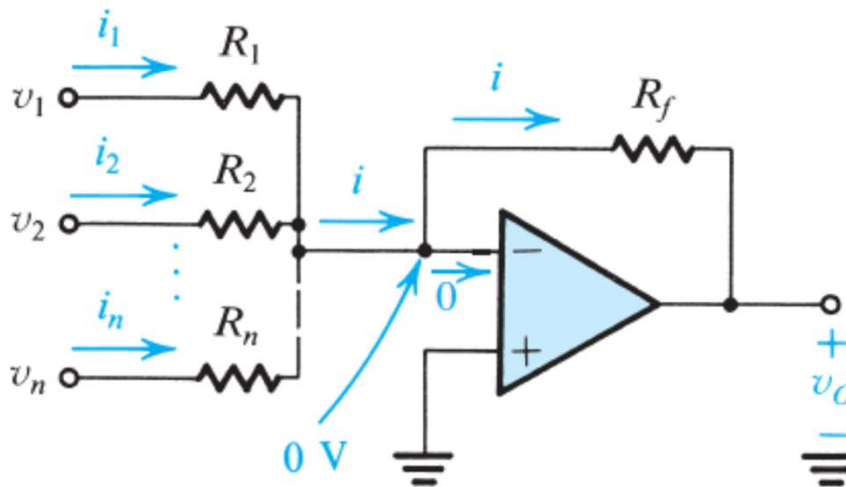


$$v_O = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \cdots + \frac{R_f}{R_n} v_n \right)$$

Summing signals with opposite sign


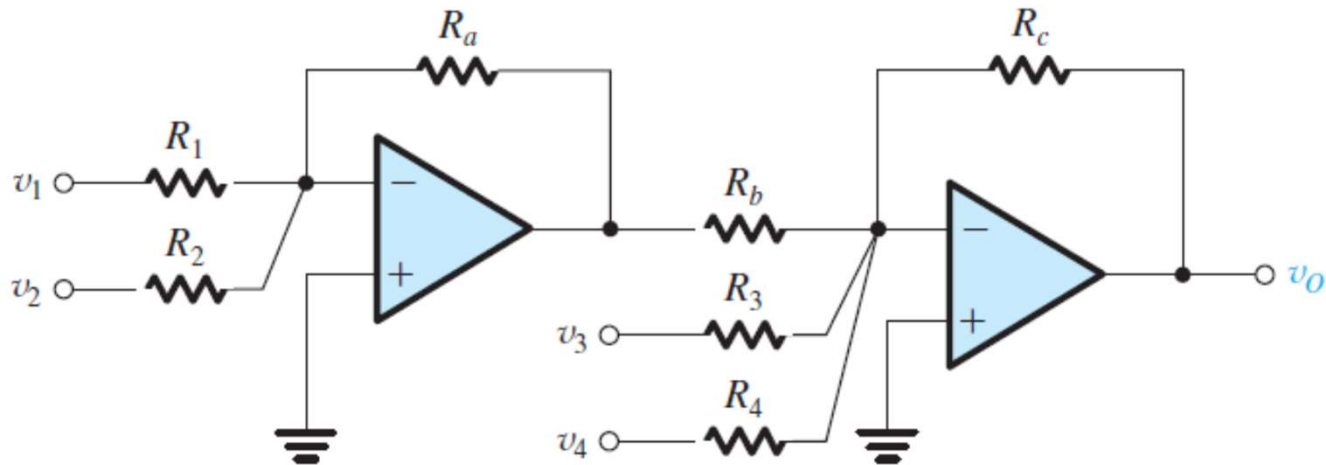


$$v_O = v_1 \left(\frac{R_a}{R_1} \right) \left(\frac{R_c}{R_b} \right) + v_2 \left(\frac{R_a}{R_2} \right) \left(\frac{R_c}{R_b} \right) - v_3 \left(\frac{R_c}{R_3} \right) - v_4 \left(\frac{R_c}{R_4} \right)$$

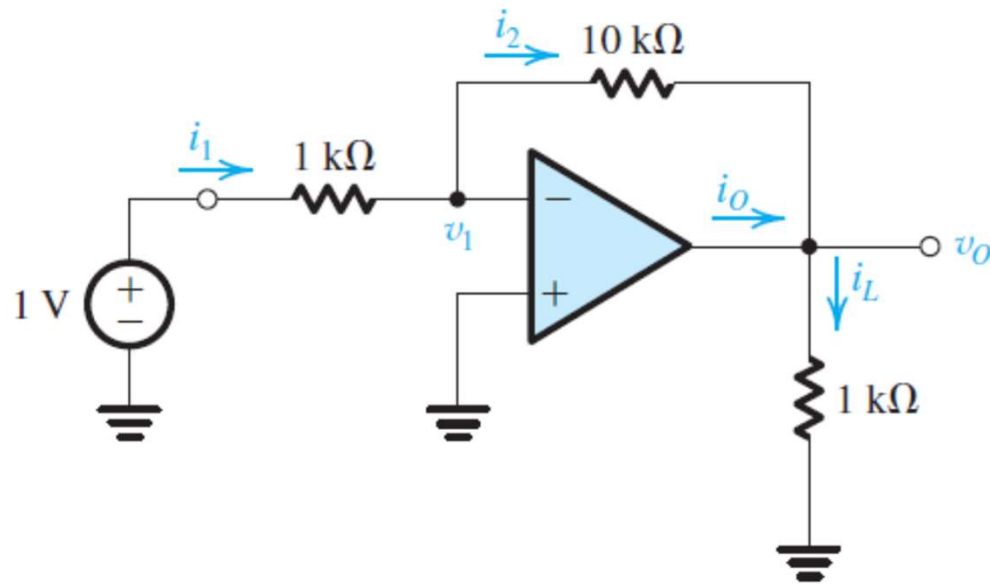Determine the values of v_1 , i_1 , i_2 , v_o , i_L , and i_o . Also determine the values of V_o/V_I , I_L/i_1 and power gain P_o/P_i





Noninverting Configuration

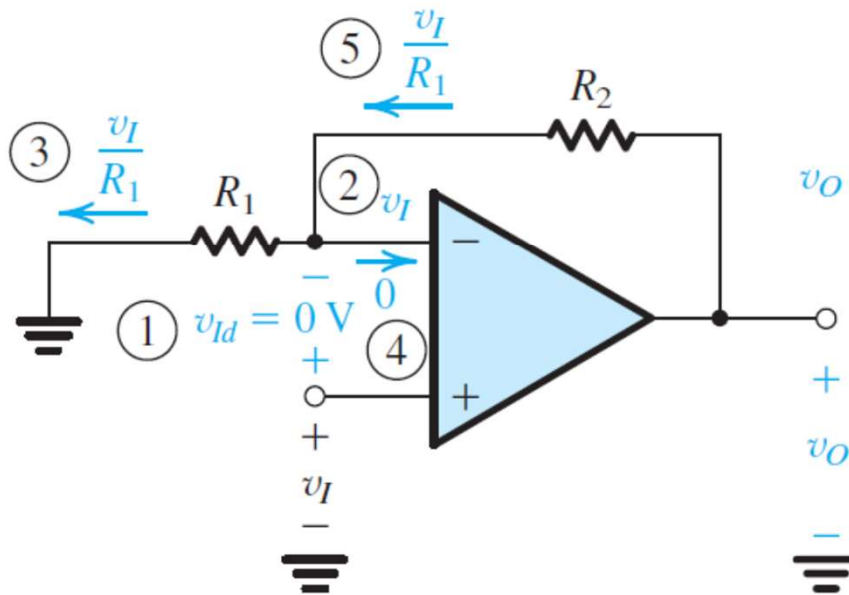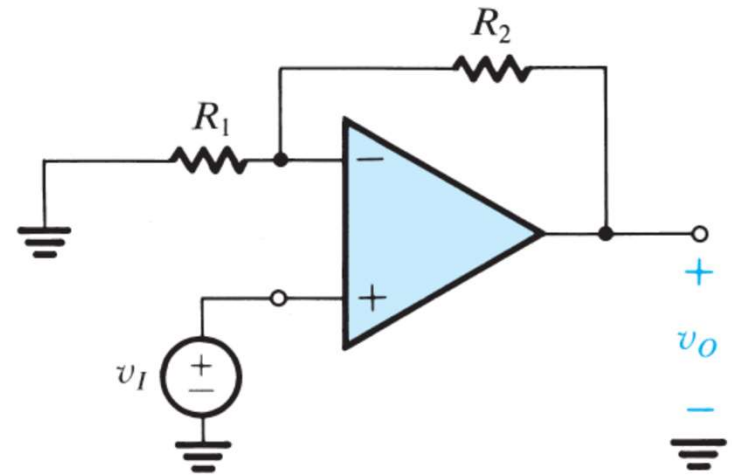


$$v_O = v_I + \frac{v_I}{R_1} R_2 = v_I \left(1 + \frac{R_2}{R_1} \right) \quad (6)$$

Application: Voltage follower

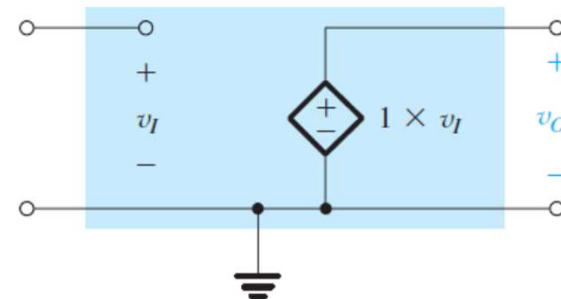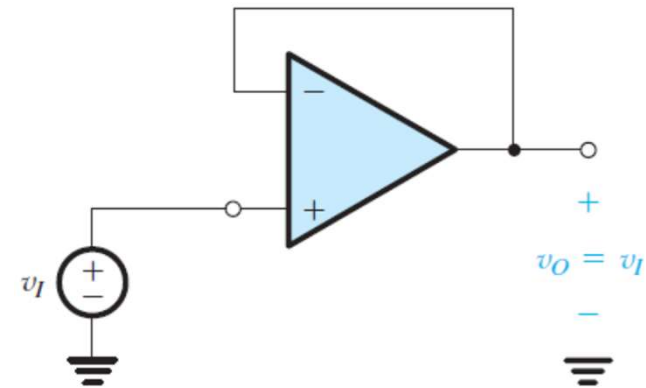- High input impedance is a desirable feature of non inverting configuration.
- Unity-gain amplifier or Voltage follower.
- Used as an impedance transformer.




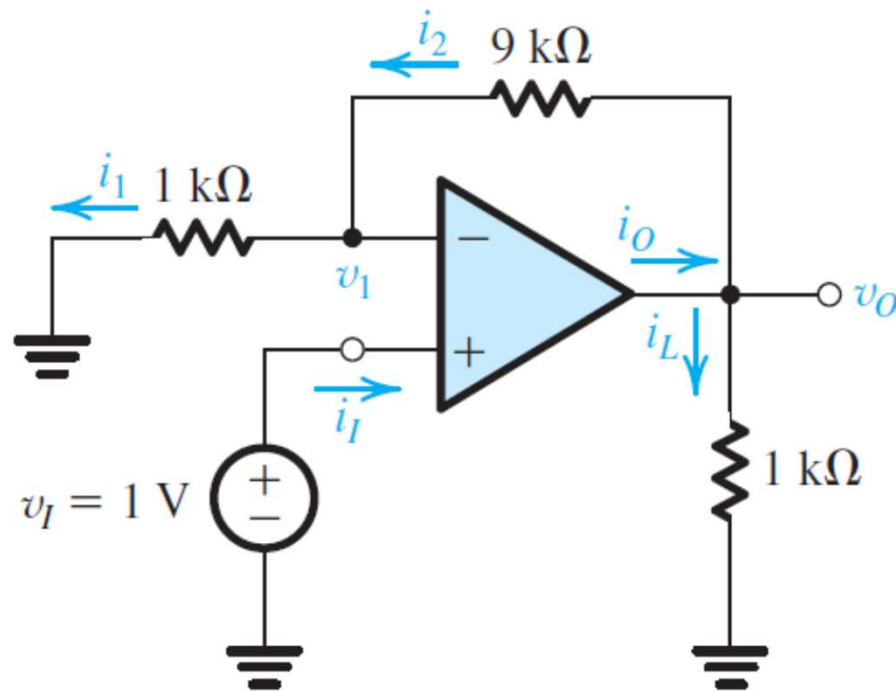Determine the values of i_I , v_1 , i_1 , i_2 , v_o , i_L , and i_o . Also determine the values of V_o/V_I , I_L/i_I and power gain P_L/P_I



Difference Amplifier


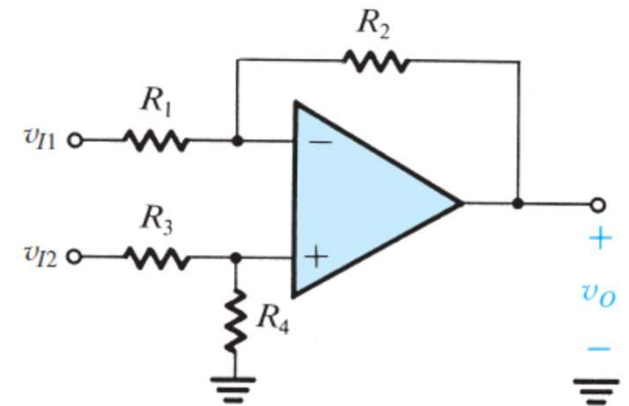
- Combination of inverting and noninverting configurations.
- Common mode signals need to be rejected, hence the magnitude of the inverting and noninverting must be same.
- Hence attenuate the gain of the +ve path from $(1+R_2/R_1)$ to R_2/R_1 .



$$\frac{R_4}{R_4 + R_3} \left(1 + \frac{R_2}{R_1} \right) = \frac{R_2}{R_1}$$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1}$$

- By Superposition:

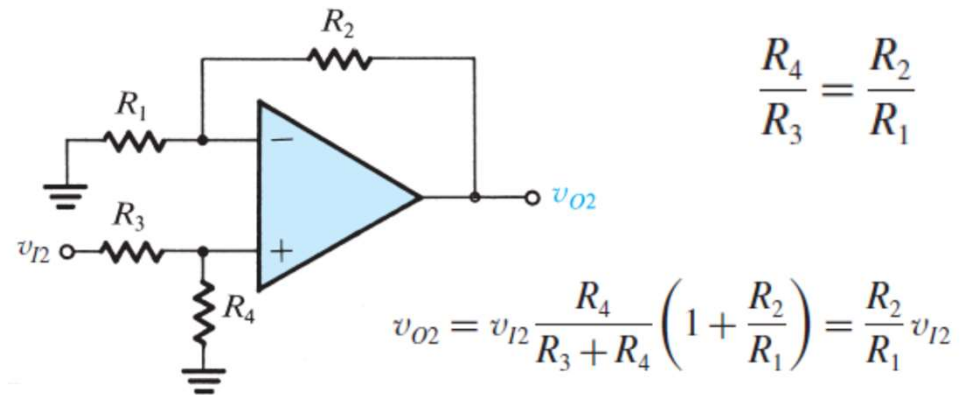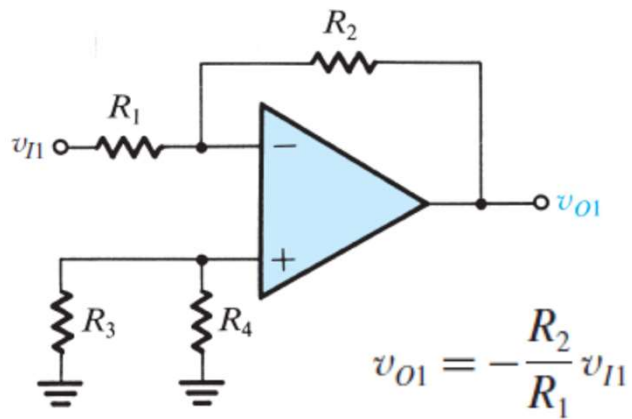


$$v_O = \frac{R_2}{R_1} (v_{I2} - v_{I1}) = \frac{R_2}{R_1} v_{Id}$$

$$A_d = \frac{R_2}{R_1}$$

$$R_3 = R_1 \quad \text{and} \quad R_4 = R_2$$

- Use superposition to determine V_o

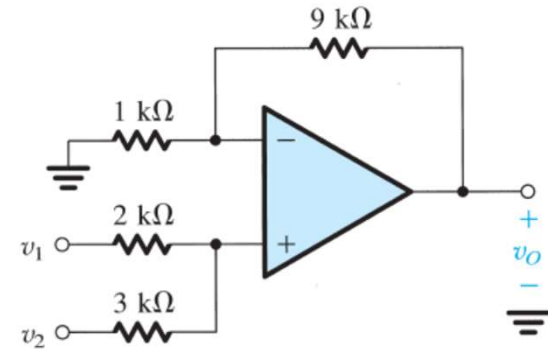

$$v_o = 6v_1 + 4v_2$$

- If the 1K resistor is disconnected from the ground and connected to V_3 , determine V_o .

$$v_o = 6v_1 + 4v_2 - 9v_3$$

- Design a non inverting amplifier with a gain of 2. At the maximum output voltage of 10 V the current in the voltage divider is to be 10 μ A.

$$v_0 = 10 \text{ V}$$

$$\frac{v_0 - v_1}{R_2} = 10 \text{ } \mu\text{A}$$

$$G = 2 = 1 + R_2/R_1$$

$$\frac{v_1}{R_1} = 10 \text{ } \mu\text{A}$$

$$R_1 = 0.5 \text{ M}\Omega$$

$$R_1 = R_2$$


$$v_o = 2v_1$$

$$v_1 = 5 \text{ V}$$


Instrumentation Amplifier

- To address the low input resistance of the difference amplifier.

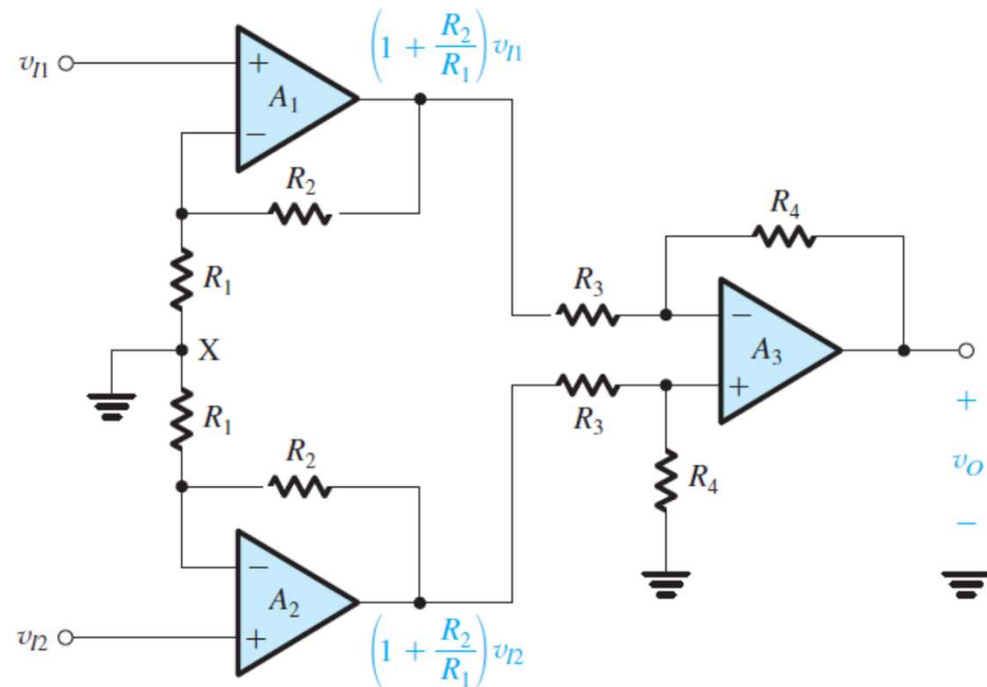
$$v_O = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1} \right) v_{Id}$$



Instrumentation Amplifier

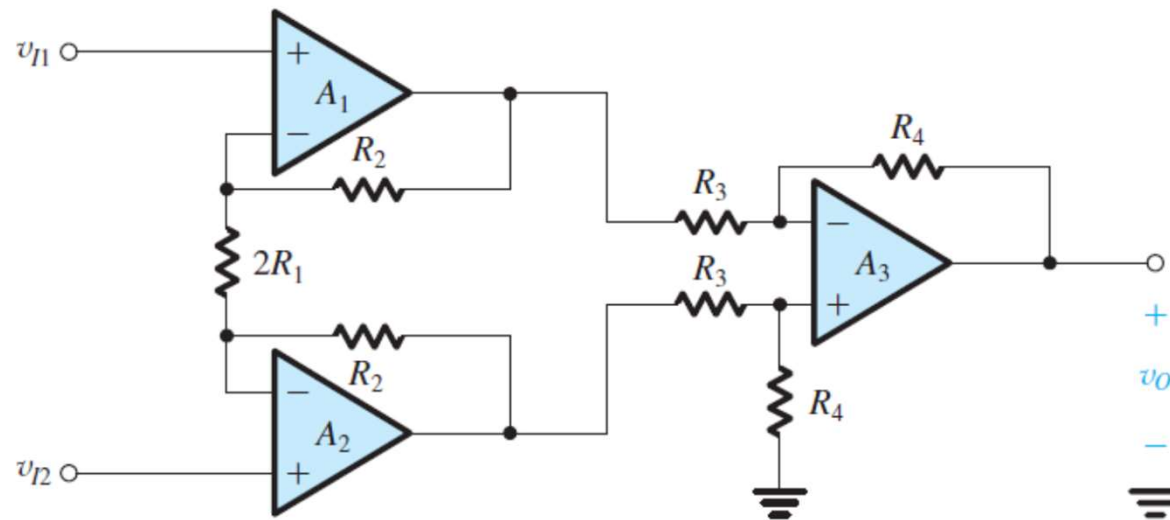

Instrumentation Amplifier

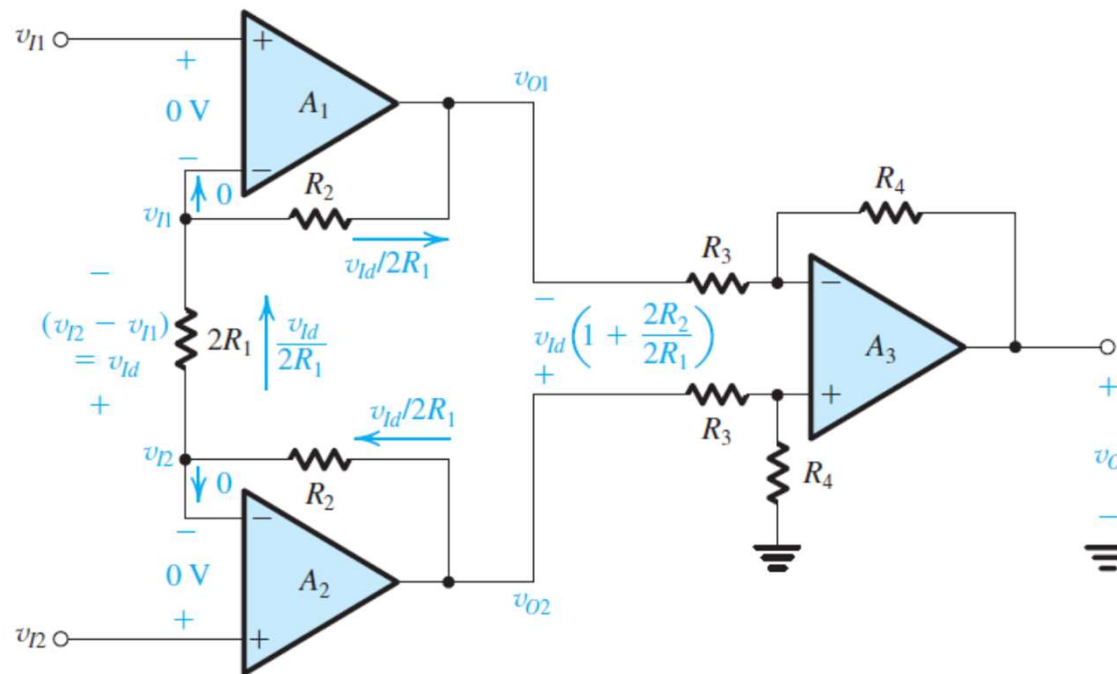

$$v_{O2} - v_{O1} = \left(1 + \frac{2R_2}{2R_1}\right) v_{Id}$$

$$A_d \equiv \frac{v_O}{v_{Id}} = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right)$$

$$v_O = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) v_{Id}$$

$$A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2 + R'_2}{2R_1}\right)$$